

①

[illegible]

-II Zener Diode Voltage Regulator

function of a voltage regulator is to provide a constant low ripple output voltage under varying load current conditions. Very high quality voltage regulators are available in integrated circuits, at times it may be sufficient and convenient to use a Zener diode as voltage regulator in simple power supplies and as voltage references in more complex power supplies for other applications. Since the Zener diode will conduct in the reverse direction for any output voltage V_o greater than V_Z , the Zener diode will not exceed V_Z at normal conditions. As the load current I_L changes, the Zener diode will conduct sufficient current to maintain a voltage drop of $(V_S - V_o)$ across the series dropping resistor, R_S . The selected Zener diode must have a reverse breakdown voltage equal to the desired output voltage V_o and be capable of dissipating the power that results when R_L is open. The difference between V_S and V_o should be selected as small as possible but must be large enough to prevent the voltage drop across R_S from exceeding $(V_S - V_o)$, when I_L is maximum. It is clear that a smaller value for R_S means a smaller value for $(V_S - V_o)$; however, a smaller value for R_S will result in a greater diode current when R_L is large and this increases the power dissipation requirement of the diode. Since the load is in parallel with the Zener diode, the voltage across R_L is always the same as across Zener diode and is $V_Z = \text{constant Zener voltage}$. The supply voltage V_S must be greater than V_Z . Zener diode **MUST** be operated under load. If not, the Zener is still delivering power (more than usual) to the load.

FIGURE

Construct the circuit shown in Figure 3. By using **5.1V** Zener diode. (Make sure the diode is connected with correct polarity).

Set the correct setting of the DMMs to measure V_S , V_o and I_S .

Ask the Teacher to inspect your circuit.

Adjust the DC power supply output adjustment potentiometer fully counter clock wise, and switch it ON. (Set $V_S = 0V$.)

Adjust the voltage source (V_S) corresponding to Table 2. Use the DMM to measure the load voltage V_o and record it in Table-2. Then Calculate I_L , I_Z and P_Z


where $I_L = V_o / R_L$, $I_Z = I_S - I_L$ and $P_Z = I_Z \times V_Z$.

When finished, set the (V_S) to $0.0V$.

Observe what happens to V_o and why.

Calculate the percentage voltage regulation (V.R %) of your circuit, and record it in Table 2.

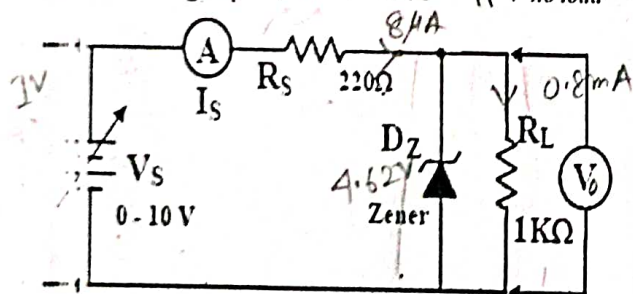Use the following equation: $V.R \% = ((V_{no\ load} - V_{full\ load}) / V_{full\ load}) \times 100\%$



1. Zener diode voltage regulator with variable power supply.

2. Zener diode voltage regulator with variable power supply data.

V_S	V_o	1.0	2.0	3.0	4.0	5.0	6.0	7.0	8.0	9.0	10.0
V_o	(V)	0.824	1.667	2.58	3.29	4.62	4.62	4.62	4.62	4.62	4.62
I_S	(mA)	0.824	1.7	2.0	3.3	4.84	6.6	10	14.5	19.9	23.1
I_L	(mA)	0.824	0	0	0	4.62	4.62	4.62	4.62	4.62	4.62
I_Z	(mA)	0	0	0	0	0.002	1.58	5.38	9.88	14.33	18.56
P_Z	(mW)	0	0	0	0	0.009					
V_R	(V)	21.36	19.97	18.58	21.9	0	0	0	0	0	0

1. What is the difference between p-n Junction diode and zener diode?
2. What is break down voltage?
3. What are the applications of Zener diode?
4. What is cut-in-voltage?
5. What is voltage regulator?

$$q = V/R$$