

Answers

4) ac load  $\delta (R_{AC}) = R_C \parallel R_L$

$$= \frac{2 \times 0.5}{2 + 0.5}$$

$$= \frac{1}{2.5} \text{ k}\Omega$$

Voltage gain =  $\beta \times \frac{R_{AC}}{R_{in}}$

$$= 50 \times \frac{1/2.5}{1}$$

$$= \frac{50}{2.5}$$

$$= 20$$

~~so  $\delta V_o = 20 \times 20$~~

~~∴  $V_o = 20 \times 20$~~

$\therefore$  Voltage gain = 20

7)



$$I_1 = I_{EF} - 5 \text{ mA}$$

$$I = \frac{I_1}{1 + 2/\beta}$$

$$= \frac{5}{1 + \frac{2}{50}}$$


$$= 4.8 \text{ mA}$$

10)  $V(B) = V_{cc} \times \frac{R_2}{R_1 + R_2}$

$$= 25 \times \frac{2.2}{(10 + 2.2)}$$

$$= 4.5 \text{ V}$$

$$V(BE) = 0.2 \text{ V}$$

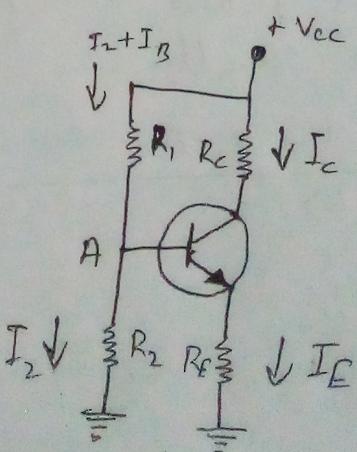

Name → Partha Banjjee Roll No. → 21F80032 Page → 2

$$V(BE) = V(B) - V(E)$$

$$\Rightarrow 0.7 = 4.5 - V(E)$$

$$\Rightarrow V(E) = 3.8 \text{ V}$$

18) Power gain = current gain × voltage gain  
=  $132 \times 145$   
=  $19140 \text{ W}$

$$A_P = \frac{P_{out}}{P_{in}}$$

$$\Rightarrow 19140 = \frac{P_{out}}{32 \times 10^{-6}}$$

$$\Rightarrow P_{out} = 0.61 \text{ W}$$

9)  $A = 100$   
 $R_i = 10 \text{ k}\Omega$   
 $R_o = 20 \text{ k}\Omega$   
 $\beta = 0.1$

$$R_{if} = 10 \times (1 + (0.1 \times 100)) \\ = 110 \text{ k}\Omega$$

$$R_{of} = \frac{R_o}{1 + A\beta} \\ = \frac{20}{11} = 1.81 \text{ k}\Omega$$

17)  $S = 50$

$$\Delta I_{co} = 1 \mu\text{A}$$

$$\therefore S = \frac{I_c}{\Delta I_{co}}$$

$$I_c = 50 \Delta I_{co}$$

$$= 50 \times 1$$

$$= 50 \mu\text{A}$$

Name → Partha Banerjee Roll No → 21F80032 Page → 3

2) Gain-bandwidth product is always constant

$$\Rightarrow \mu = \frac{4a \times 10^6}{40} \\ = 10^5 \text{ Hz} \\ = 100 \text{ kHz}$$

14)  $V_R = 2V_P$  Diode in conduction  $\cancel{-/-}$   
 $V_R = 2V_P$  No diode in parallel  $\cancel{-/-}$

15)  $A = 90$   
 $B = 0.005$   $A_P A_{op} = 0.45$

$$A_f = \frac{A}{1 + BA} \\ = \frac{90}{1 + (0.005 \times 90)} \\ = 62.06$$