

## EES51: Electrical Technology Lab

**Title:** To perform the open circuit test and short circuit test on a single-phase transformer

### Expt. 4: Tests on 1 $\Phi$ Transformer

#### Electrical Power: Requirements

- ✓ Fluorescent Lamp
- ✓ Television
- ✓ Music System
- ✓ Battery Charger
- ✓ Rechargeable Torchlight
- ✓ Toaster
- ✓ Water Pump
- ✓ Electric Water Geyser
- ✓ Electric iron
- ✓ Air conditioner
- ✓ Air heater
- ✓ Refrigerator
- ✓ Cooking Heater
- ✓ Mixer Grinder
- ✓ Hair Dryer
- ✓ Electric Saver








### Expt. 4: Tests on 1 $\Phi$ Transformer

#### Electrical Power: Generation
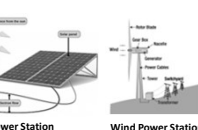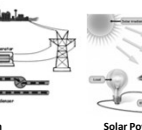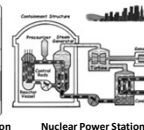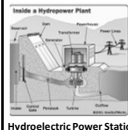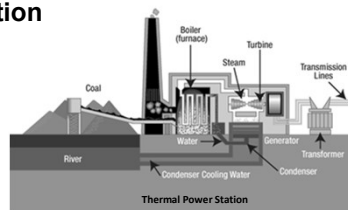
##### □ Electrical Power Station

- Thermal
- Hydroelectric
- Nuclear
- Non-Conventional




### Expt. 4: Tests on 1 $\Phi$ Transformer

#### Electrical Power: G to U
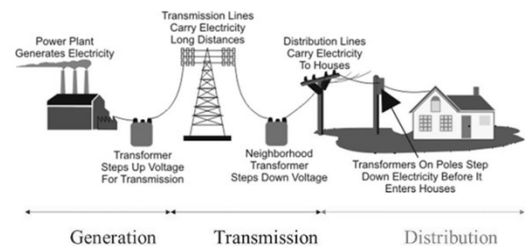
##### □ Electrical Power

- Generation
- Transmission
- Distribution
- Utilization




### Expt. 4: Tests on 1 $\Phi$ Transformer

#### Electrical Power: G to U
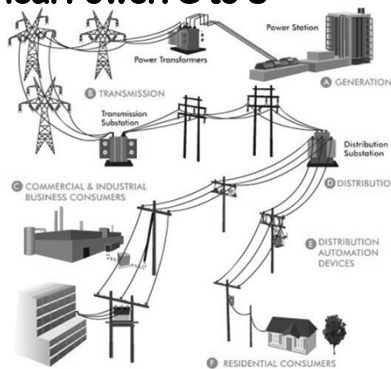
##### □ Electrical Power


- Generation
- Transmission
- Distribution
- Utilization



### Expt. 4: Tests on 1 $\Phi$ Transformer


#### Electrical Power: G to U
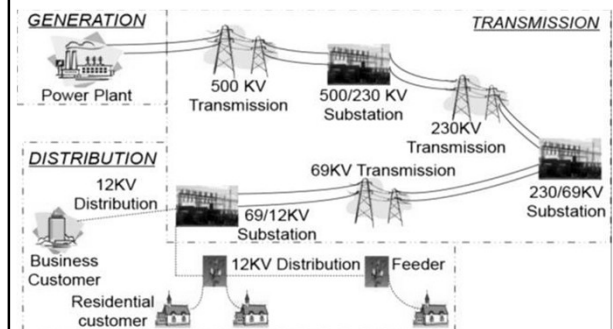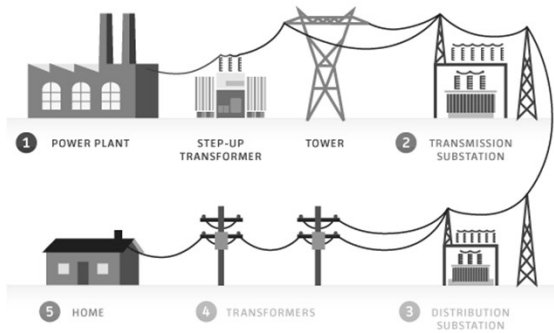
##### □ Electrical Power

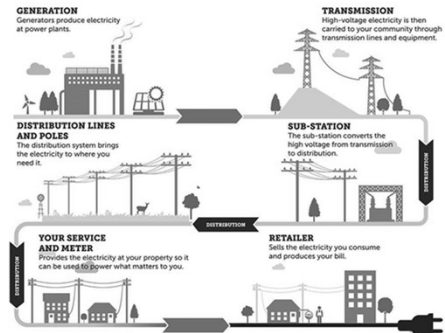


Expt. 4: Tests on 1 $\Phi$  Transformer


## Electrical Power: G to U

☐ Electrical PowerExpt. 4: Tests on 1 $\Phi$  Transformer

## Electrical Power: G to U

☐ Electrical PowerExpt. 4: Tests on 1 $\Phi$  Transformer

## Electrical Power: G to U

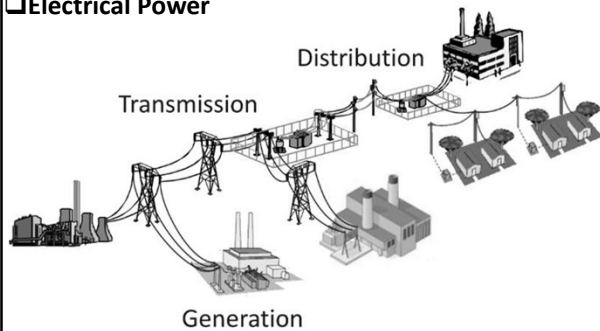
☐ Electrical PowerExpt. 4: Tests on 1 $\Phi$  Transformer

## Electrical Power: G to U

☐ Electrical Power

## A.C POWER TRANSMISSION

## COMPLETE EXPLANATION

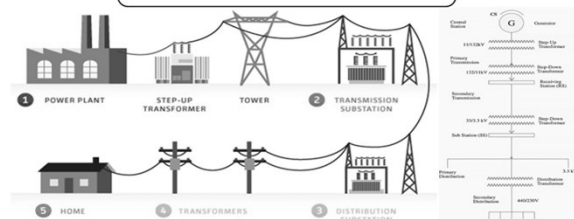Expt. 4: Tests on 1 $\Phi$  Transformer

## Electrical Power: G to U


☐ Electrical Power

- ☐ Generation
- ☐ Transmission
- ☐ Distribution
- ☐ Utilization

$$P = VI$$

$$\text{For a constant amount of } V \propto 1/I$$

$$\text{Loss} = I^2R$$

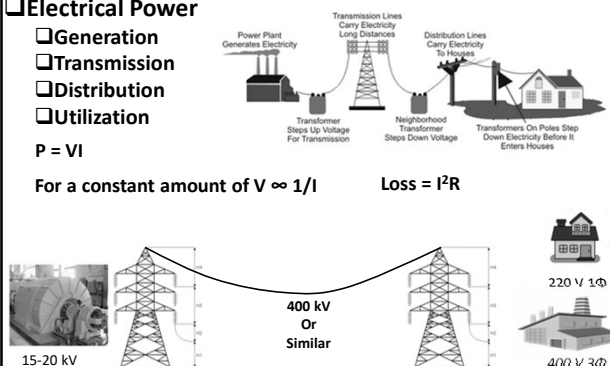Expt. 4: Tests on 1 $\Phi$  Transformer


## Transformer: Where do we see these?

Vary of forms



## Expt. 4: Tests on 1Φ Transformer


Transformer: How does it look?

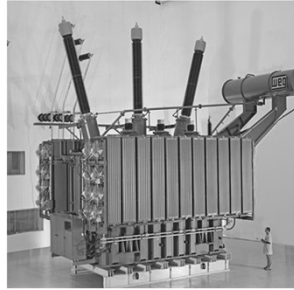
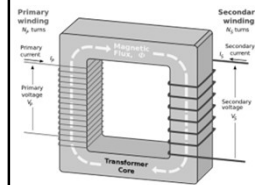
## Expt. 4: Tests on 1Φ Transformer

What is a Transformer?

Transformers are static electrical machines which are used to transfer the alternating electrical power from one circuit to another circuit with a required change in the voltage and current levels keeping the power and frequency unchanged.



Generally,


- Voltage Changes
- Current Changes
- Frequency does not change
- Power does not change (rather reduced due to losses)

## Expt. 4: Tests on 1Φ Transformer

Transformers Construction

Transformers are developed with copper windings wound over a magnetic core.

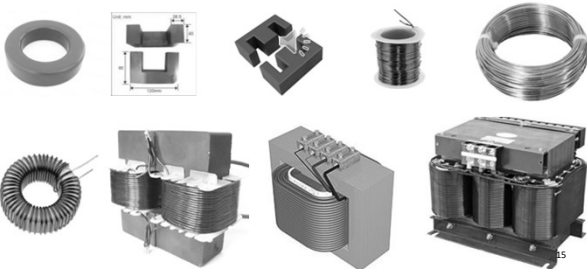- Core must be magnetic
- Copper wires are preferred for high conductivity and high ductility




## Expt. 4: Tests on 1Φ Transformer

Transformers Construction: Laminated Iron Core

Transformers are developed with copper windings wound over a soft iron core (preferably CRGO).

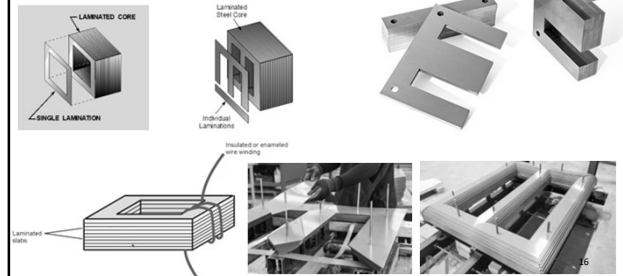- Core is laminated
- Copper wires are insulated



## Expt. 4: Tests on 1Φ Transformer

Symbols and Names


- Single Phase Transformers are represented as two inductive coils separated by two parallel lines representing the magnetic coupling.

➤ Transformer Names: According to voltage variation

- ❖ Step Up Transformer
- ❖ Step Down Transformer
- ❖ Isolation (1:1) Transformer

➤ Winding Names

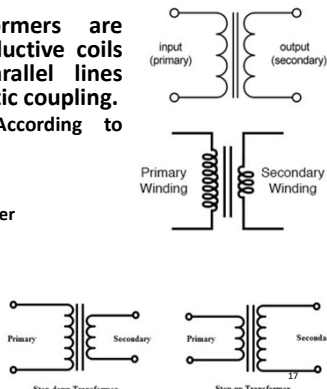
- ❖ As per the connections
  - ✓ Primary
  - ✓ Secondary
- ❖ As per the number of turns
  - ✓ HV
  - ✓ LV


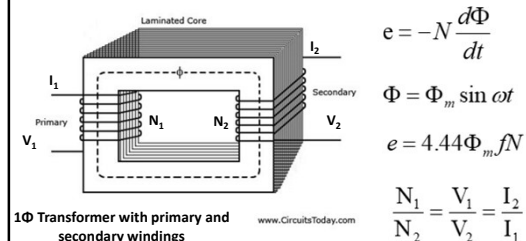
## Expt. 4: Tests on 1Φ Transformer

Operation of Transformer

- Transformer works as per the Faraday's electromagnetic induction principle.
- For an alternating current excitation, at the primary alternating flux is produced.
- Time varying flux links with both the winding and induce emf which is proportional to the number of turns.



1Φ Transformer with primary and secondary windings

www.CircuitsToday.com

$$e = -N \frac{d\Phi}{dt}$$

$$\Phi = \Phi_m \sin \omega t$$

$$e = 4.44 \Phi_m f N$$

$$\frac{N_1}{N_2} = \frac{V_1}{V_2} = \frac{I_2}{I_1}$$

18

### Expt. 4: Tests on 1Φ Transformer

#### ❑ Losses in the Transformers


- There are two major types of losses are found in the transformers:

##### ❖ Iron Loss

- Eddy Current Loss
- Hysteresis Loss
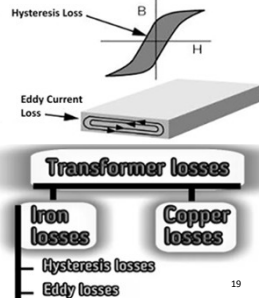
##### ❖ Copper Loss

- Primary copper loss
- Secondary copper loss





19

### Expt. 4: Tests on 1Φ Transformer
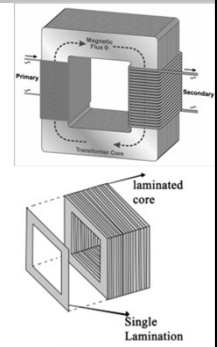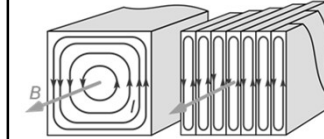
#### • Eddy Current Loss:

- Whenever the magnetic flux linking to conducting material changes, voltages are induced in all possible paths and hence the induced currents called eddy currents are set up throughout the volume of the conducting material.
- The electrical energy which is wasted in the form of heat due to eddy currents in the core material is called eddy current loss.



$$R = \frac{\rho L}{A}$$

$\rho$  = resistivity  
 $L$  = length  
 $A$  = cross sectional area

20

### Expt. 4: Tests on 1Φ Transformer

#### • Eddy Current Loss:


- Depends on the thickness.

$$R = \frac{\rho L}{A}$$


$\rho$  = resistivity  
 $L$  = length  
 $A$  = cross sectional area



**Solid core**

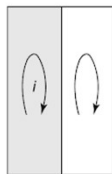

**Thick lamination**

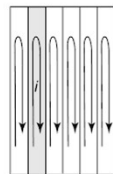

**Thin lamination**



**Decreasing eddy losses**

21

### Expt. 4: Tests on 1Φ Transformer

- Eddy Current Loss,  $P_e = K_e B_{\max}^2 f^2 t^2 V$  watts


Where  $K_e$  = constant

$B_{\max}$  = maximum flux density in Tesla

$f$  = frequency of magnetic reversal in Hz

$t$  = thickness of laminations in mm

$V$  = volume of core in  $m^3$

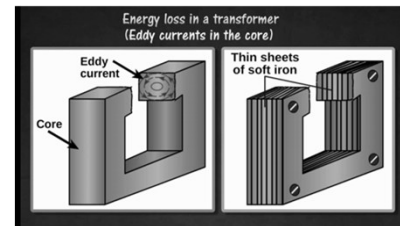

22

### Expt. 4: Tests on 1Φ Transformer

#### • Hysteresis :

##### MAGNETIC HYSTERESIS

Magnetizing force,  $H$  in a material is a magnetomotive force per unit length of the material. Unit : ampere – turns per meter (At/m)

Equation:

$$H = \frac{F_m}{l}$$

$F_m$  = magnetomotive force  
 $H$  = magnetizing force  
 $l$  = length of material

$$F_m = NI \longrightarrow H = \frac{NI}{l}$$

$H$  is depends on the number of turns of the coil of wire , current through coil, length of material.

23

### Expt. 4: Tests on 1Φ Transformer

#### • Hysteresis :

##### Magnetomotive Force

- The MMF is generated by the coil
- Strength related to number of turns and current, Symbol  $F$ , measured in Ampere turns (At)

$$F = NI$$

$$\Phi = \frac{NI}{\mathfrak{R}}$$

### Expt. 4: Tests on 1Φ Transformer

#### • Hysteresis :

#### MAGNETIC FIELD STRENGTH, H (MAGNETISING FORCE)

- Defined as magnetomotive force,  $F_m$  per metre length of measurement being ampere-turn per metre.


$$H = \frac{F_m}{l} = \frac{NI}{l}$$

Labels in diagram: magnetomotive force ( $F_m$ ), number of turns ( $N$ ), Current ( $I$ ), average length of magnetic circuit ( $l$ ).

25

### Expt. 4: Tests on 1Φ Transformer


#### • Hysteresis :

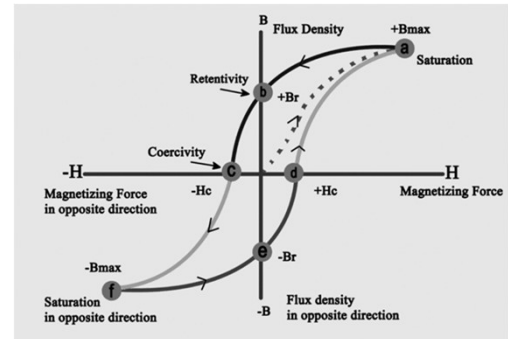

26

### Expt. 4: Tests on 1Φ Transformer

#### • Hysteresis :

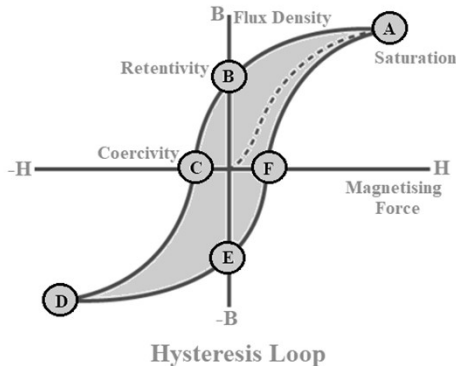

27

### Expt. 4: Tests on 1Φ Transformer

#### • H

#### Relationship between B-H

- Flux density ( $B$ ) and magnetizing force ( $H$ ) are related by the equation

$$B = \mu H$$

However, relative permeability is  $\mu_r = \frac{\mu}{\mu_0} \Rightarrow \mu = \mu_r \mu_0$

So,  $B = \mu H = \mu_r \mu_0 H$

$B$  = flux density,  $Wb / m^2$  or  $T$

$H$  = magnetizing force,  $At/m$

$\mu$  = permeability of the medium,  $Wb / At.m$

$\mu_0$  = permeability of free space,  $Wb / At.m$


$\mu_r$  = relative permeability

$\mu_0$ , permeability of free space is given as  $4\pi \times 10^{-7} Wb/At.m$

### Expt. 4: Tests on 1Φ Transformer


#### • Hysteresis :
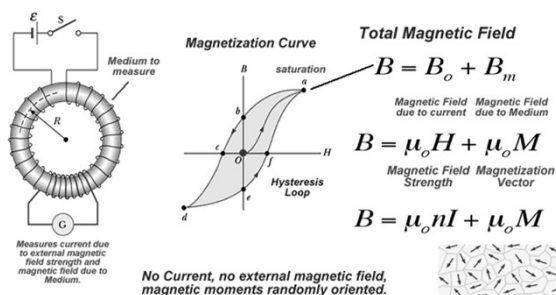
#### Magnetic Field Strength and Magnetization Vector



### Expt. 4: Tests on 1Φ Transformer


#### • Hysteresis :

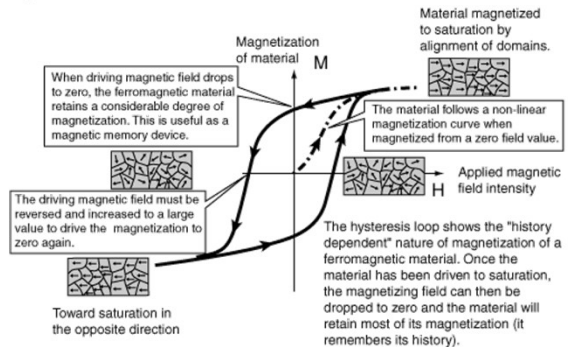

30

### Expt. 4: Tests on 1Φ Transformer

#### • Hysteresis :

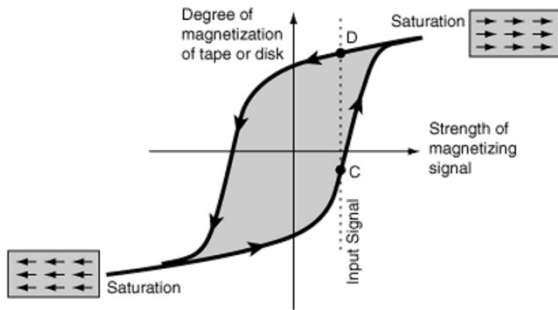


31

### Expt. 4: Tests on 1Φ Transformer
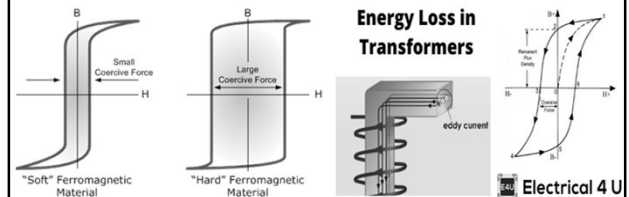
#### • Hysteresis loss:

- The lag or delay of a magnetic material known commonly as **Magnetic Hysteresis**, relates to the magnetization properties of a material by which it firstly becomes magnetized and then demagnetized.




32
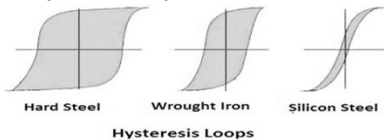
### Expt. 4: Tests on 1Φ Transformer

Hysteresis loss,  $P_h = \dot{\eta} B_{\max}^{1.6} f V$  watts,

- Where  $B_{\max}$  = maximum flux density in Tesla,
- $f$  = frequency of magnetic reversal in Hz,
- $= NP/120$  where  $N$  is in r.p.m,
- $V$  = volume of the core material in  $m^3$
- $\dot{\eta}$  = Steinmetz hysteresis coefficient.
- It can be proved that **the energy lost per unit volume of material in a complete cycle of magnetization is equal to the area of the hysteresis loop.**



33

### Expt. 4: Tests on 1Φ Transformer

Hysteresis loss,  $P_h = \dot{\eta} B_{\max}^{1.6} f V$  watts,

- Where  $B_{\max}$  = maximum flux density in Tesla,
- $f$  = frequency of magnetic reversal in Hz,
- $= NP/120$  where  $N$  is in r.p.m,
- $V$  = volume of the core material in  $m^3$
- $\dot{\eta}$  = Steinmetz hysteresis coefficient.
- It can be proved that **the energy lost per unit volume of material in a complete cycle of magnetization is equal to the area of the hysteresis loop.**

34

### Expt. 4: Tests on 1Φ Transformer

TABLE I  
CHARACTERISTICS OF ELECTRICAL STEEL SHEETS

Material	50A1300	50A470	20RMHF1200
Grade	Low	Middle	High
Thickness $h$ (mm)	0.5	0.5	0.2
Conductivity $\sigma$ (S/m)	$7.14 \times 10^6$	$2.56 \times 10^6$	$1.96 \times 10^6$
$K_v$	$3.10 \times 10^{-4}$	$1.10 \times 10^{-4}$	$3.04 \times 10^{-5}$
$K_h$	$6.01 \times 10^{-3}$	$2.71 \times 10^{-2}$	$1.53 \times 10^{-3}$
$\kappa$	0.82	0.96	1.94

35

<https://ieeexplore.ieee.org/stamp/stamp.jsp?arnumber=5512834>

### Expt. 4: Tests on 1Φ Transformer

TABLE IV  
SPECIFICATIONS OF IRON CORE (M47)

Parameter	Value	Description
$K_h$	273.2	Hysteresis loss factor
$K_e$	0.4786	Eddy current loss factor
$d_t$	0.65 mm	Lamination thickness
$\rho_{fe}$	390 nΩm	Resistivity
$\alpha$	1.2558	MSE constant
$\beta$	1.685	MSE constant

36

<https://ieeexplore.ieee.org/stamp/stamp.jsp?tp=&arnumber=6584731>


## EES51: Electrical Technology Lab

**Title: To perform the open circuit test and short circuit test on a single-phase transformer**

### Expt. 4: Tests on 1 $\Phi$ Transformer

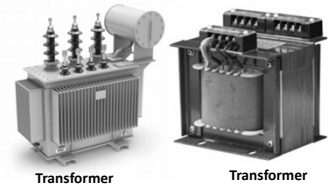
#### What is a Transformer?

Transformers are static electrical machines which are used to transfer the alternating electrical power from one circuit to another circuit with a required change in the voltage and current levels keeping the power and frequency unchanged.



Transformer

Transformer

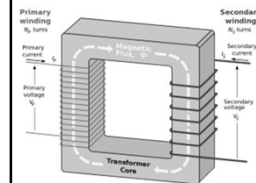


Generally,

- Voltage Changes
- Current Changes
- Frequency dose not change
- Power dose not change (rather reduced due to losses)

38

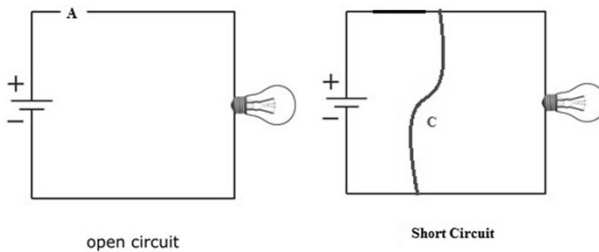
### Expt. 4: Tests on 1 $\Phi$ Transformer



<https://www.marinesite.info/2017/06/circuit-faults-open-circuit-short-circuit-Earth-Fault.html>

39
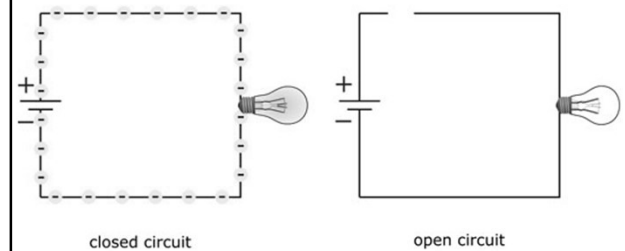
### Expt. 4: Tests on 1 $\Phi$ Transformer



<https://www.marinesite.info/2017/06/circuit-faults-open-circuit-short-circuit-Earth-Fault.html>


40

### Expt. 4: Tests on 1 $\Phi$ Transformer

#### Transformer: Open and Short Circuit
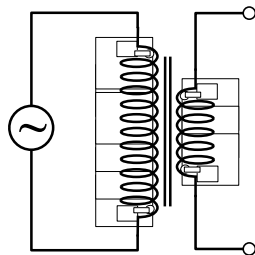
##### • Transformer: Open circuit condition

- Power will applied at the primary side.
- No load will be connected.
- No power will be taken from the secondary.
- Input power = Losses of the transformer (Iron Losses).




### Expt. 4: Tests on 1 $\Phi$ Transformer

#### Transformer: Open and Short Circuit

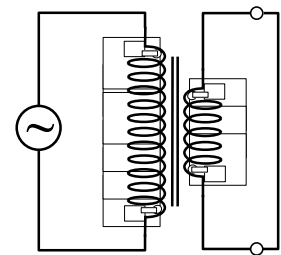
##### • Transformer: Short circuit condition

- Power will applied at the primary side.
- No load will be connected.
- But the secondary terminal will be shorted.
- No power will be taken from the secondary.
- Input power = Losses of the transformer (Copper Losses).




### Expt. 4: Tests on 1 $\Phi$ Transformer

- Panel Board (Backside)

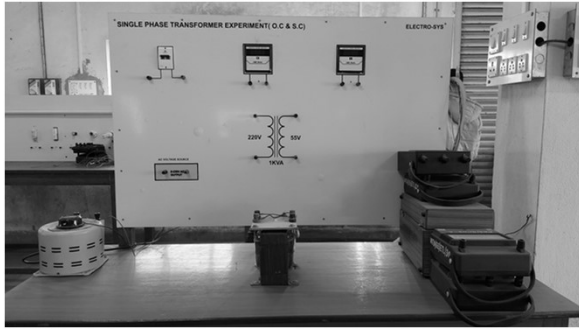


### Expt. 4: Tests on 1 $\Phi$ Transformer

- Panel Board (Backside)

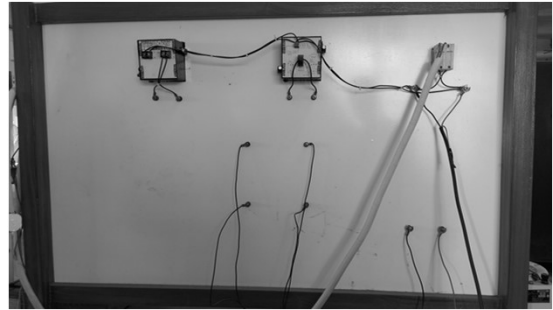


### Expt. 4: Tests on 1 $\Phi$ Transformer

- Variac

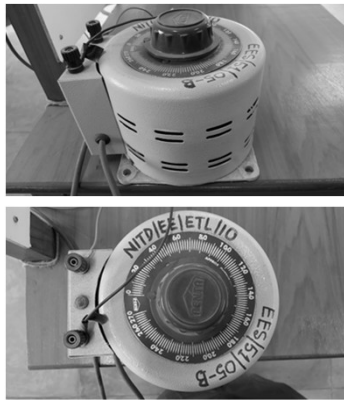



### Expt. 4: Tests on 1 $\Phi$ Transformer

- Variac

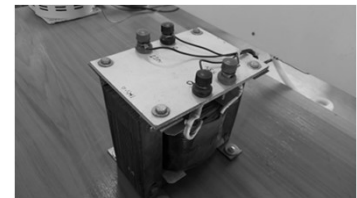
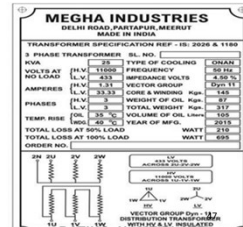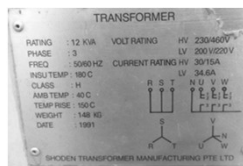
### Expt. 4: Tests on 1 $\Phi$ Transformer

- Transformer Ratings
  - Rated Power (kVA)
  - Rated Voltage (Volts)
  - Rated Current (Amps)
  - Rated Frequency (Hz)



### Expt. 4: Tests on 1 $\Phi$ Transformer

#### Transformer Used: 1 $\Phi$ Transformer

☐ Name Plate: 1 kVA, 55/230 V, 50 Hz 1  $\Phi$  Transformer...


- |                         |   |
|-------------------------|---|
| Rated Power             | = 01 kVA = 1000 VA                      |
| Rated Primary Voltage   | = 55 V                                  |
| Rated Secondary Voltage | = 230 V                                 |
| Rated Primary Current   | = $1000/55 \text{ A} = 18.18 \text{ A}$ |
| Rated Secondary Current | = $1000/230 \text{ A} = 4.35 \text{ A}$ |
| Rated Frequency         | = 50 Hz                                 |



### Expt. 4: Tests on 1 $\Phi$ Transformer
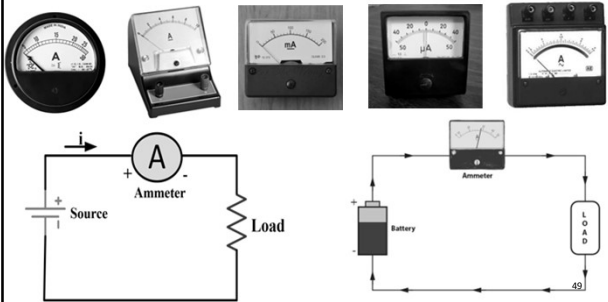
#### Measuring Instruments: Ammeter


- Ammeter measures current
- Ammeter is connected in series



### Expt. 4: Tests on 1 $\Phi$ Transformer
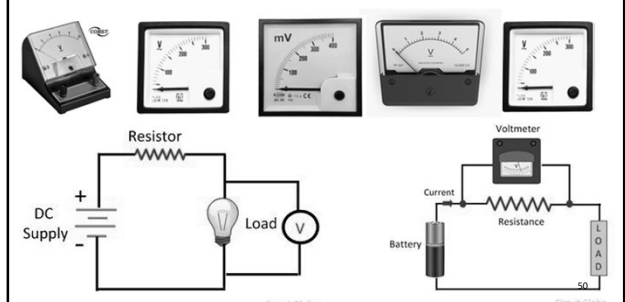
#### Measuring Instruments: Voltmeter


- Voltmeter measures voltage
- Voltmeter is connected in parallel



### Expt. 4: Tests on 1 $\Phi$ Transformer
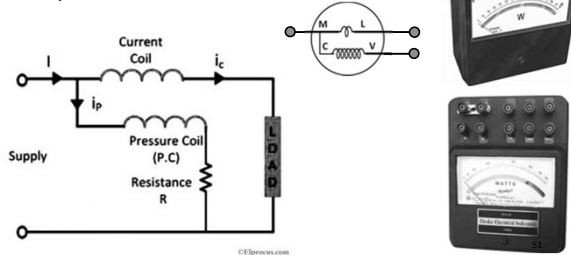
#### Measuring Instruments: Wattmeter


- Wattmeter measures the power.
- Wattmeter is operated by connecting the current coil in series and pressure/voltage coil in parallel.



### Expt. 4: Tests on 1 $\Phi$ Transformer
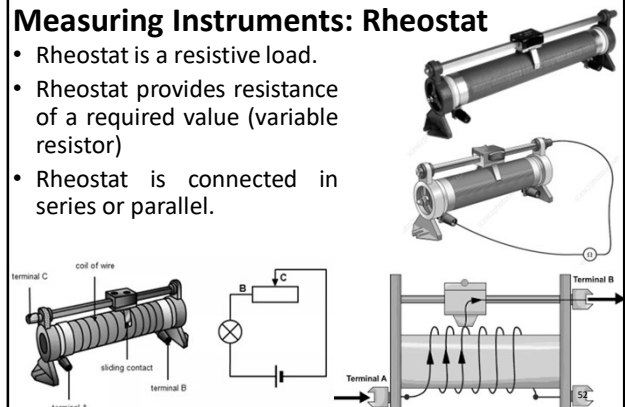
#### Measuring Instruments: Rheostat


- Rheostat is a resistive load.
- Rheostat provides resistance of a required value (variable resistor)
- Rheostat is connected in series or parallel.



### Expt. 4: Tests on 1 $\Phi$ Transformer
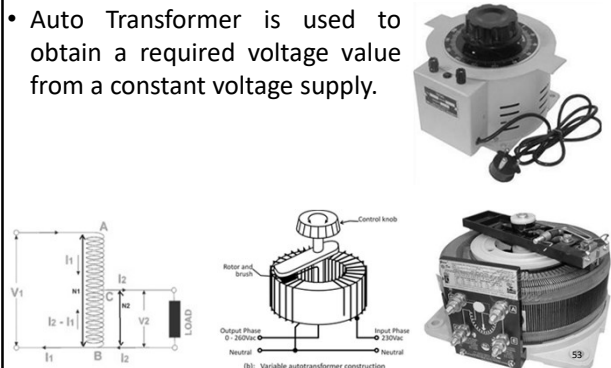
#### Measuring Instruments: Auto Transformer


- Auto Transformer is used to obtain a required voltage value from a constant voltage supply.



### Expt. 4: Tests on 1 $\Phi$ Transformer
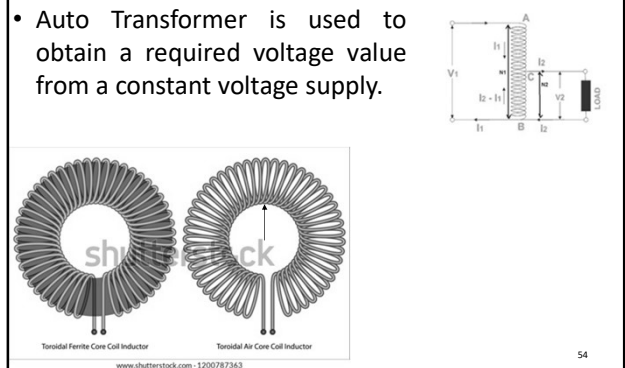
#### Measuring Instruments: Auto Transformer

- Auto Transformer is used to obtain a required voltage value from a constant voltage supply.




### Expt. 4: Tests on 1 $\Phi$ Transformer
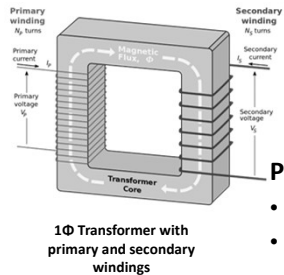
#### What are the tests?

Two tests are conducted:

- Open Circuit Test (OCT)
- Short Circuit Test (SCT)



Please remember


- OCT: HV side is kept open
- SCT: LV side is short circuited

55

### Expt. 4: Tests on 1 $\Phi$ Transformer
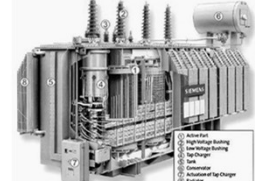
#### • Why OCT and SCT?


- Open and short circuit tests are performed on a transformer to determine the:
  - Losses and Efficiency of transformer
  - Equivalent circuit of transformer
  - Voltage regulation of transformer



56
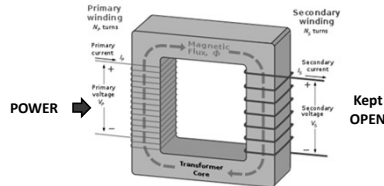
### Expt. 4: Tests on 1 $\Phi$ Transformer

- **PURPOSE OF OCT:** To find the core loss or iron loss
- The main purpose of this test are
  - To find the iron loss
  - To calculate no load current
  - To calculate the core loss resistance ( $R_0$ )
  - To calculate the magnetizing reactance ( $X_0$ ).
- In O.C. test LV winding is connected to a.c. supply, keeping HV open (though the reverse is also possible).




- Note: Sometimes a voltmeter may be connected across secondary as voltmeter resistance is very high & voltmeter current is negligibly small so that secondary is treated as open circuit.

### Expt. 4: Tests on 1 $\Phi$ Transformer
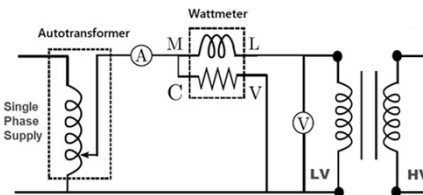
#### • Open Circuit Test on Transformer


- The connection diagram for open circuit test on transformer is shown in the figure.
- A voltmeter, wattmeter, and an ammeter are connected in LV side of the transformer as shown.
- The voltage at rated frequency is applied to that LV side with the help of a variac of variable ratio auto transformer.



58
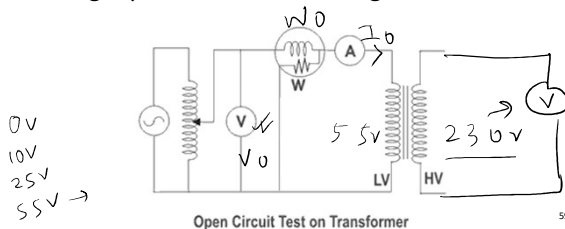
### Expt. 4: Tests on 1 $\Phi$ Transformer

- **Open Circuit Test on Transformer**
- With the help of variac, applied voltage gets slowly increased in different steps and the voltage ( $V_0$ ) current ( $I_0$ ) and power ( $W_0$ ) until the voltmeter gives reading equal to the rated voltage of the LV side.




59

### Expt. 4: Tests on 1 $\Phi$ Transformer
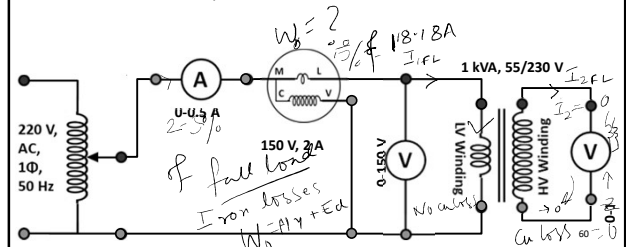
#### CIRCUIT CONNECTION

- **Open Circuit Test: HV Winding is kept Open Circuited.**
- Take the transformer and keep the HV side open.
- Connect primary winding with the output from a variac.
- Connect Ammeter, Voltmeter and Wattmeter as shown.



### Expt. 4: Tests on 1Φ Transformer

#### □ OCT Test Procedure: Step by Step

- 1) Connect the circuit as shown in circuit diagram.
- 2) Switch on the supply after checking connection by concerned teacher.
- 3) Increases the input voltage the to the transformer winding up to **rated value (230V) slowly using dimmer stat.**
- 4) Measure the primary voltage, primary current, primary circuit power and secondary voltage of transformer.
- 5) Reduce the voltage slowly using Variac.
- 6) Switch off the supply and remove connections.

### Expt. 4: Tests on 1Φ Transformer

#### • OCT: Important Observations

- Ammeter gives the reading of the no load current ( $I_0$ ).
- Transformer no load current is always very small, 2 to 5 % of its full load current.
- $I_1 = I_0$  is very low hence copper losses on primary are also very low.
- As secondary (HV winding) is open, ie,  $I_2 = 0$ , hence secondary copper losses are zero.
- Thus the total copper losses in O.C. test are negligibly small, hence neglected (**No Copper Loss in OCT**).
- **Therefore the wattmeter reading in O.C. test gives iron losses (which remain constant for all the loads).**

62

### Expt. 4: Tests on 1Φ Transformer

#### • OCT Equivalent Circuit: No-Load Condition

##### • Equivalent Circuit:

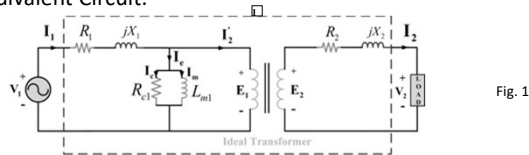


Fig. 1

##### • Equivalent Circuit (Referred to primary):

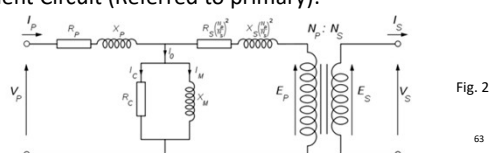


Fig. 2

63

### Expt. 4: Tests on 1Φ Transformer

#### • OCT Equivalent Circuit: No-Load Condition

- No-Load current is 2-5% of the full load current
- As no load current  $I_0$  is quite small compared to rated current of the transformer, the voltage drops due to this current that can be taken as negligible.

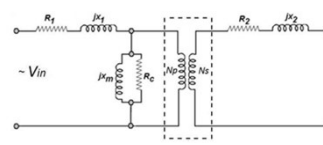


Fig. 1


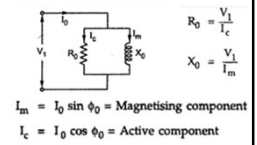


Fig. 2

64

### Expt. 4: Tests on 1Φ Transformer

#### No load equivalent circuit:

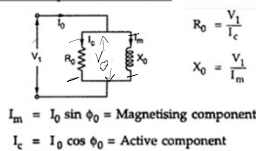

$$I_m = I_0 \sin \phi_0 = \text{Magnetising component}$$

$$I_c = I_0 \cos \phi_0 = \text{Active component}$$

- Now we know  $W_o$ ,  $V_o$  and  $I_o$

$$W_o = V_o I_o \cos \Phi_o \quad \text{Or} \quad \cos \Phi_o = \frac{W_o}{V_o I_o}$$

$$\text{Now, } I_c = I_o \cos \Phi_o \quad \text{and} \quad I_m = I_o \sin \Phi_o$$

$$\text{Thus, } R_c = R_o = \frac{V_o}{I_c} \quad \text{and} \quad X_m = X_o = \frac{V_o}{I_m}$$


65

### Expt. 4: Tests on 1Φ Transformer

#### Transformer: Open and Short Circuit
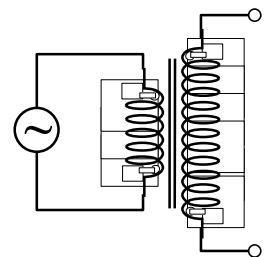
##### • Transformer: Open circuit condition

- Power will applied at the primary side.
- No load will be connected.
- No power will be taken from the secondary.
- Input power = Losses of the transformer (Iron Losses).




### Expt. 4: Tests on 1 $\Phi$ Transformer

#### Transformer: Open and Short Circuit
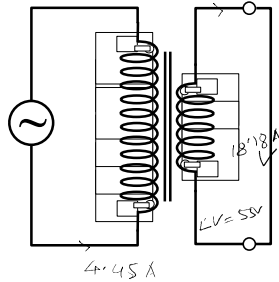
##### • Transformer: Short circuit condition


- Power will applied at the primary side.
- No load will be connected.
- But the secondary terminal will be shorted.
- No power will be taken from the secondary.
- Input power = Losses of the transformer (Copper Losses).



### Expt. 4: Tests on 1 $\Phi$ Transformer
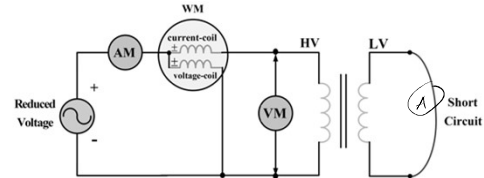
#### • Short Circuit Test on Transformer

- The main purpose of this test is
  - to find full load copper loss
  - winding parameters ( $R_{eq}$  &  $X_{eq}$ )




- In this test, secondary (LV) is short circuited.
- As secondary is shorted, on rated primary voltage it draws a large amount of current.
- Such large current can cause overheating and burning of the transformer.

### Expt. 4: Tests on 1 $\Phi$ Transformer
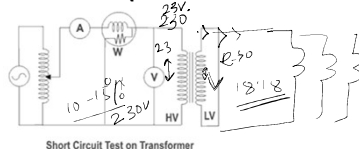
#### • SCT on Transformer


- Power is supplied to the HV side with LV side shorted.
- Voltmeter, ammeter and wattmeter are connected in HV side.
- A low voltage (10-15% of rated voltage) is applied to the HV (primary in this condition) side.
- Now with the help of variac applied voltage is slowly increased until the ammeter gives reading equal to the rated current of the HV side (i.e. 4.35 A not 18.18 A).



### Expt. 4: Tests on 1 $\Phi$ Transformer
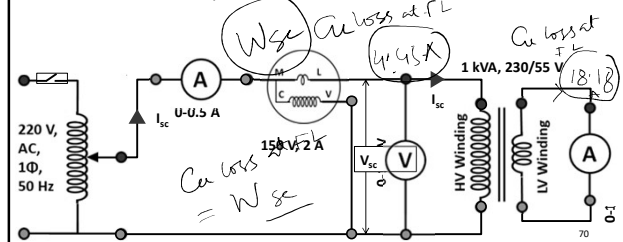
#### CIRCUIT CONNECTION

- **Short Circuit Test: Low Voltage Winding is Short Circuited**
- Take the transformer and keep the LV side short circuited.
- Connect the variac output to the primary winding (HV) .
- Connect Ammeter, Voltmeter and Wattmeter as shown.



### Expt. 4: Tests on 1 $\Phi$ Transformer

#### • SCT on Transformer: Procedures

##### • Procedure: S.C. test:

- 1) Connect the circuit as shown in circuit diagram.
- 2) Switch on the supply after checking connection by concerned teacher.
- 3) Increases the input voltage very carefully and slowly using dimmer stat so that the current in secondary winding reaches rated value.
- 4) The readings of the Voltmeter ( $V_{sc}$ ), Ammeter ( $I_{sc}$ ) and Watt-meter ( $W_{sc}$ ) are noted.
- 5) Reduce the voltage slowly using dimmer stat.
- 6) Switch off the supply and remove connections.

### Expt. 4: Tests on 1 $\Phi$ Transformer


#### • SCT on Transformer: Observations

- To limit this short circuit current, primary is supplied with low/reduced voltage (10 – 15 % of the rated voltage) which is just enough to cause rated current to flow through primary which can be observed on an ammeter.
- As the applied voltage is low the iron loss will be low and neglected.
- Since the currents flowing through the windings are rated currents hence the wattmeter reading is the power loss which is equal to full load copper losses.

### Expt. 4: Tests on 1Φ Transformer

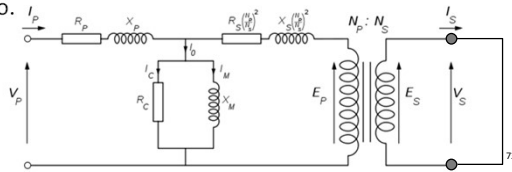
#### SCT on Transformer: Equivalent Circuit

- SCT data is also used to obtain the parameters to approximate the equivalent circuit of a transformer.
- These values are referred to the HV side of the transformer as the test is conducted on the HV side of the transformer.
- These values could easily be converted to the LV side by dividing these values with the square of transformation ratio.



### Expt. 4: Tests on 1Φ Transformer
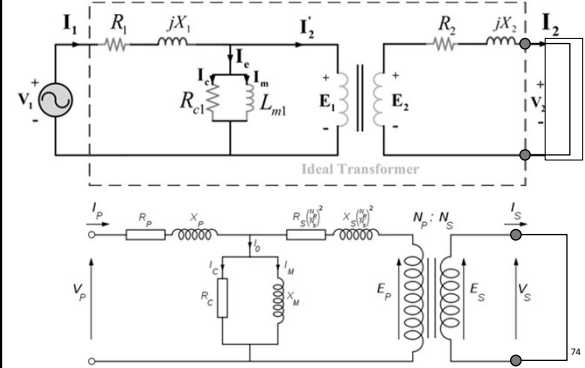
#### SCT on Transformer: Equivalent Circuit



### Expt. 4: Tests on 1Φ Transformer

#### SCT on Transformer: Equivalent Circuit

- As the core loss is negligible in the SCT, the equivalent circuit reduces to:

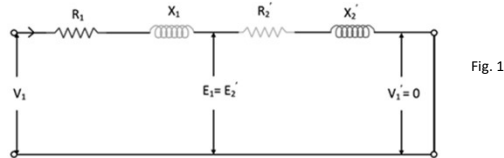


Fig. 1

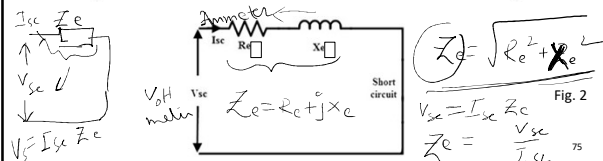


Fig. 2

### Expt. 4: Tests on 1Φ Transformer

#### SCT on Transformer: Calculations

- In SCT, the wattmeter reading can be taken as equal to copper losses in the transformer. Let us consider wattmeter reading is  $W_{sc}$ .

$$W_{sc} = R_e I_{sc}^2$$

- Where,  $R_e$  is equivalent resistance of transformer.
- If,  $Z_e$  is equivalent impedance of transformer.

$$Z_e = \frac{V_{sc}}{I_{sc}}$$

- Therefore, if equivalent reactance of transformer is  $X_e$ .

$$X_e = \sqrt{Z_e^2 - R_e^2}$$

75

### Expt. 4: Tests on 1Φ Transformer


- Calculation of Efficiency

#### What is the Efficiency of Transformer?

$$\eta = \frac{\text{output power}}{\text{input power}} = \frac{\text{output power}}{\text{output power} + \text{losses}}$$

$$\eta = \frac{\text{output power}}{\text{output power} + \text{iron losses} + \text{copper losses}}$$
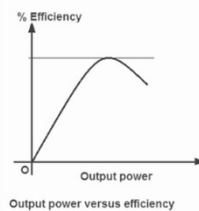
$$\eta = \frac{V_2 I_2 \cos \phi_2}{V_2 I_2 \cos \phi_2 + P_i + P_c}$$



Output power versus efficiency

$$\% \text{ efficiency} = \frac{kVA \text{ rating} \times 10^3 \times p.f.}{kVA \text{ rating} \times 10^3 \times p.f. + W_{cu} + W_i} \times 100$$

77

### Expt. 4: Tests on 1Φ Transformer

- Voltage Regulation

- The **voltage regulation** of the transformer is the percentage change in the output **voltage** from no-load to full-load.
- Voltage regulation** is represented as a fraction of either **no-load** or **full load voltage**.
- Since power factor is a determining factor in the secondary **voltage**, power factor influences **voltage regulation**.

$$VR = \frac{\text{No - Load Voltage} - \text{Full Load Voltage}}{\text{No - Load Voltage}} \times 100\% \quad \text{Or} \quad VR = \frac{E_2 - V_2}{E_2} \times 100\% \quad \text{VR-Down} \checkmark$$

$$VR = \frac{\text{No - Load Voltage} - \text{Full Load Voltage}}{\text{Full - Load Voltage}} \times 100\% \quad \text{Or} \quad VR = \frac{E_2 - V_2}{V_2} \times 100\% \quad \text{VR-Up}$$

78

### Expt. 4: Tests on 1 $\Phi$ Transformer

#### EXPERIMENTAL RESULTS:

Table-I: For O.C. test:

Sl. No	Primary Voltage ( $V_1$ )	No-load current ( $I_0$ )	Secondary voltage ( $V_2$ )	Wattmeter reading ( $W_{sc}$ )
1.				
2.				
3.				
4.				
5.				

Table-II: For S.C. test:

Sl. No	Primary Voltage ( $V_{sc}$ )	Primary current ( $I_{sc}$ )	Wattmeter reading ( $W_{sc}$ )
1.			
2.			
3.			
4.			
5.			

79

### Expt. 4: Tests on 1 $\Phi$ Transformer

#### APPARATUS USED:

SL. No	Equipment	Specification	Makers	Quantity
1.	Auto Transformer			
2.	Ammeter			
3.	Volt Meter			
4.	Watt Meter			
5.				
6.				
7.				

80

### Expt. 4: Tests on 1 $\Phi$ Transformer

- **Report:**
- Calculate the equivalent circuit parameters and draw that circuit.
- Calculate efficiency of the transformer.
- **Precautions:**
- On short circuit test the supply voltage should be applied through an autotransformer and increased very slowly from its zero value, so that rated current flows through the circuit.
- Current should not exceed rated value otherwise damage may occur.
- The short circuiting copper wire should be of a larger cross section than that used in transformer winding and all connections must be clean and tight.

81

### Expt. 4: Tests on 1 $\Phi$ Transformer

- **Questions:**
- State the losses occurring in a transformer at no-load and on what these depend.
- If a transformer rated for 50 c/s is worked on 60 c/s will the losses increase or decrease for the same applied voltage.
- What materials are used for construction of core?
- What are the different types of core sections used for transformer construction?
- Why the core is laminated in a transformer?
- A transformer is rated 3 KVA, 230/110-V, 50 HZ. What will be the effect on its magnetizing current, if it is now connected to 230-V, 25 HZ supply voltage?
- What is the purpose of short-circuit test on a transformer/
- Why it is necessary to apply low voltage to one side of the transformer when performed short-circuit test?
- Why iron- losses are not considered in short- circuit calculation?

82

### Expt. 4: Tests on 1 $\Phi$ Transformer

#### Transformer Components?

Transformers are static electrical devices which are used to transfer alternating electrical power from one circuit to another circuit with a desired change in the voltage and current levels keeping the power frequency unchanged.

#### Cooling, Monitoring, Safety

- Oil
- Radiator
- Conservator tank
- Breather
- Buchholz Relay

83


### Expt. 4: Tests on 1 $\Phi$ Transformer

#### Annexure I

84

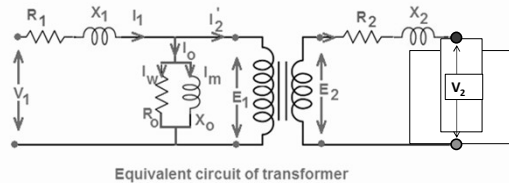
### Expt. 4: Tests on 1 $\Phi$ Transformer

- **Why Voltage Regulation is Important?**
- **Equivalent Circuit at No-Load**
- As there is no current through secondary ( $I_2 = 0$ ), there will be no drop across  $R_2$  and  $X_2$ .
- At no-load condition the output voltage  $V_2$  is equal to  $E_2$ .



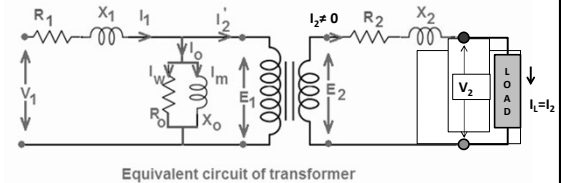
### Expt. 4: Tests on 1 $\Phi$ Transformer

- **Why Voltage Regulation is Important?**
- **Equivalent Circuit at Load**
- As soon as the load is connected across the secondary,  $I_L$  starts flowing through the load which is equal to  $I_2$ .
- Due to  $I_2$ ,  $R_2$  and  $X_2$  will develop certain amount of voltage drops across them.
- At load conditions, the output voltage  $V_2$  is less than  $E_2$ .
- With the increase in load,  $V_2$  will decrease.



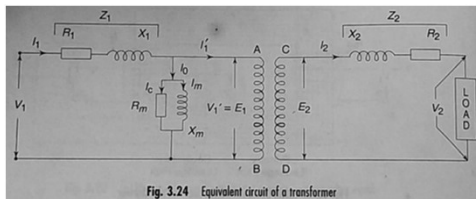
### Expt. 4: Tests on 1 $\Phi$ Transformer

- **Voltage Regulation Calculation**
- Therefore, the voltage will be varied at the output with load and other conditions.
- Thus, the concept of voltage regulation came.
- The **voltage regulation** formula can be derived from the equivalent circuit and the associated phasor diagram:



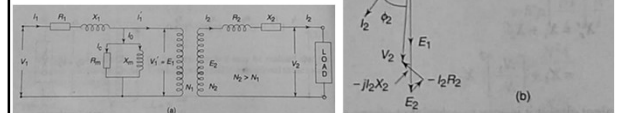
### Expt. 4: Tests on 1 $\Phi$ Transformer

- **Voltage Regulation Calculation**
- The phasor diagram of the transformer on load is:
- $N_2 > N_1$
- $E_2 > E_1$
- $V_2 > V_1$
- $I_2 < I_1$
- $V'_1 = E_1$
- $V_2 = E_2 - I_2(R_2 + jX_2)$


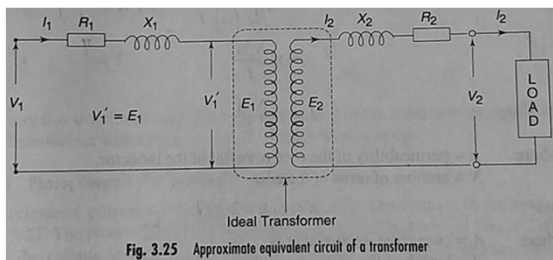
### Expt. 4: Tests on 1 $\Phi$ Transformer

- **Voltage Regulation Calculation**
- As the no-load current is very low the equivalent circuit can be approximated as:




### Expt. 4: Tests on 1 $\Phi$ Transformer

- **Voltage Regulation Calculation**
- Approximated equivalent circuit referred to the primary side is as follows:

$$R'_e = R_1 + R'_2 \quad X'_e = \left(\frac{N_1}{N_2}\right)^2 X_2$$
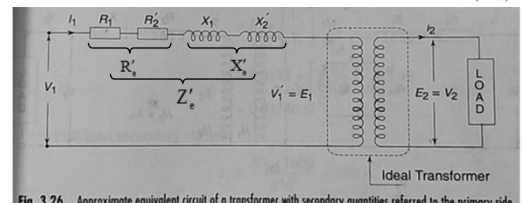
$$Z'_e = R'_e + jX'_e \quad R'_2 = \left(\frac{N_1}{N_2}\right)^2 R_2$$



### Expt. 4: Tests on 1Φ Transformer

- Voltage Regulation Calculation
- Approximated equivalent circuit referred to primary side:

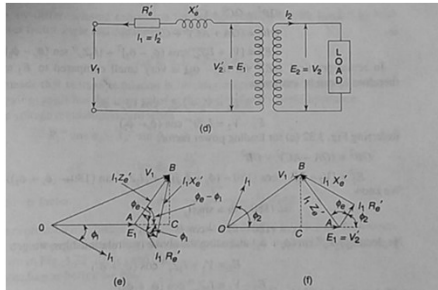


Fig. 3.32 (d) approximate equivalent circuit referred to primary side (e) corresponding phasor diagram for lagging power factor (f) corresponding phasor diagram for leading power factor

91

### Expt. 4: Tests on 1Φ Transformer

- Voltage Regulation Calculation
- Approximated equivalent circuit referred to secondary side:


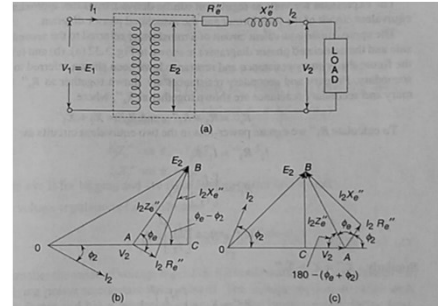


Fig. 3.32 (a) Approximate equivalent circuit referred to secondary side (b) phasor diagram for lagging power factor (c) corresponding phasor diagram for leading power factor

92
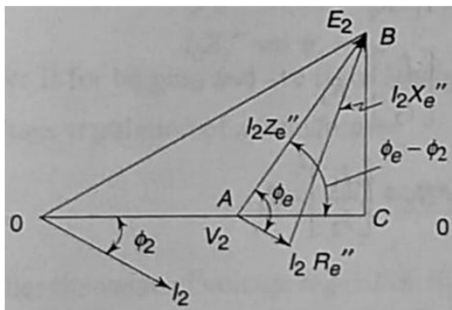
### Expt. 4: Tests on 1Φ Transformer


- Voltage Regulation Calculation
- Phasor diagram for lagging power factor



93
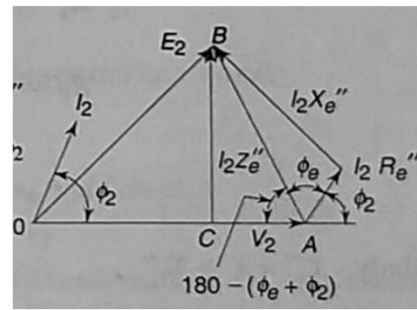
### Expt. 4: Tests on 1Φ Transformer

- Voltage Regulation Calculation
- Phasor diagram for leading power factor



94

### Expt. 4: Tests on 1Φ Transformer

- Voltage Regulation Calculation
- Now, from the equivalent circuit we can get,

$$Z_e'' = R_e'' + X_e'' \quad R_e'' = R_2 + R_1' \quad R_1' = \left(\frac{N_2}{N_1}\right)^2 R_1$$

$$X_e'' = X_2 + X_1' \quad X_1' = \left(\frac{N_2}{N_1}\right)^2 X_1$$

- Now, from the phasor diagram we can get,

$$\text{Regulation} = \frac{E_2 - V_2}{E_2} = \frac{I_2 Z_e'' \cos(\Phi_e \mp \Phi_2)}{V_2} \times 100\%$$

$$\text{Regulation} = \frac{I_2 (R_e'' \cos \Phi_2 \pm X_e'' \sin \Phi_2)}{V_2} \times 100\%$$

- Note: + for lagging p.f. and - for leading p.f.

95

### Expt. 4: Tests on 1Φ Transformer

- Voltage Regulation from SCT Data
- Now, using the equivalent circuit obtained from SCT, we can write:

$$W_{sc} = (I_{2sc})^2 R_e'' \text{ and } E_{2sc} = (I_{2sc}) Z_e''$$

$$\text{Where, } E_{2sc} = \left(\frac{N_2}{N_1}\right) E_{1sc} = \left(\frac{N_2}{N_1}\right) V_{1sc}$$

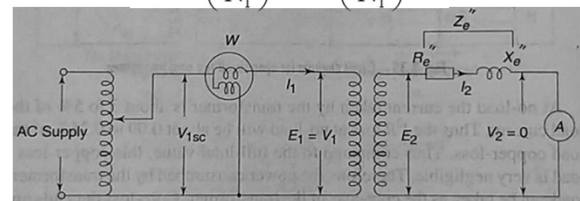


Fig. 3.37 Equivalent circuit of Fig. 3.36 with primary quantities referred to the secondary



### Expt. 4: Tests on 1Φ Transformer

- **Voltage Regulation from SCT Data**
- Now, using the equivalent circuit we can get from SCT, we can write:
 
$$R_e'' = \frac{W_{sc}}{(I_{2sc})^2} \quad \text{and} \quad Z_e'' = \frac{E_{2sc}}{I_{2sc}}$$
- Thus, we have:
 
$$X_e'' = \sqrt{(Z_e'')^2 - (R_e'')^2}$$
- Now, from SCT, we can write:
 
$$W_{sc} = E_{2sc} I_{2sc} \cos \Phi_e$$
- Thus, we have:
 
$$\cos \Phi_e = \frac{W_{sc}}{E_{2sc} I_{2sc}}$$

$$\Phi_e = \cos^{-1} \left( \frac{W_{sc}}{E_{2sc} I_{2sc}} \right)$$

### Expt. 4: Tests on 1Φ Transformer

- **Voltage Regulation from SCT Data**
  - Now, if the secondary quantities are referred to the primary, then, from SCT, we can write:
 
$$W_{sc} = V_{1sc} I_1 \cos \Phi_e$$
  - Thus, we have:
 
$$\cos \Phi_e = \frac{W_{sc}}{V_{1sc} I_1} \quad \text{Or,} \quad \Phi_e = \cos^{-1} \left( \frac{W_{sc}}{V_{1sc} I_1} \right)$$
- $$\text{Regulation} = \frac{E_2 - V_2}{E_2} = \frac{I_2 Z_e'' \cos(\Phi_e - \Phi_2)}{V_2} \times 100\%$$
- $$\text{Regulation} = \frac{E_2 - V_2}{E_2} = \frac{V_{1sc} \cos(\Phi_e - \Phi_2)}{V_2'} \times 100\%$$

### Expt. 4: Tests on 1Φ Transformer

- **Example 01:**
- A 15 kVA, 2200/220 V, 1Φ transformer gave the following test data: OCT:  $V_0$ : 220 V,  $I_0$ : 2.72 A,  $W_0$  = 185 Watt  
 SCT:  $V_{sc}$ : 112 V,  $I_{sc}$ : 6.3 A,  $W_{sc}$  = 197 Watt
- Calculate the (a) core loss, (b) full load copper loss, (c) full load efficiency at 0.85 lagging power factor, and (d) the voltage regulation at 0.8 lagging and leading power factor.
- **Answer:**
- (a) The core loss is given by: 185 W
- (b)  $I_2(\text{FL}) = I_{HV}(\text{FL})$  is given by
 
$$I_{HV}(\text{FL}) = I_2(\text{FL}) = \frac{\text{kVA}}{V_2} = \frac{15000}{2200} \text{ A} = 6.82 \text{ A}$$

### Expt. 4: Tests on 1Φ Transformer

- **Example 01:** SCT:  $V_{sc}$ : 112 V,  $I_{sc}$ : 6.3 A,  $W_{sc}$  = 197 Watt
- Therefore the full load copper loss will be given by:
 
$$W_{cu}(\text{FL}) = W_{sc} \times \left( \frac{I_{HV}(\text{FL})}{I_{sc}} \right)^2 = 197 \times \left( \frac{6.82}{6.3} \right)^2 = 231 \text{ W}$$
- (c) The full efficiency at 0.85 lagging pf will be given by:
 
$$\eta = \frac{15 \times 10^3 \times 0.85}{(15 \times 10^3 \times 0.85) + 185 + 231} \times 100\% = 96.84\%$$
- (d) The equivalent parameters referred to secondary are:
 
$$Z_e'' = \frac{V_{1sc}}{I_{1sc}} = \frac{112}{6.3} = 17.78 \Omega \quad \text{and} \quad R_e'' = \frac{W_{sc}}{(I_{1sc})^2} = \frac{197}{(6.3)^2} = 4.96 \Omega$$
- Thus,
 
$$X_e'' = \sqrt{(17.78)^2 - (4.96)^2} = 17.07 \Omega$$

### Expt. 4: Tests on 1Φ Transformer

- **Example 01:**
- Now,  $I_{HV}(\text{FL}) = I_2(\text{FL}) = I_{2\text{Rated}} = \frac{P_{\text{Rated}}}{V_2} = \frac{15 \times 10^3}{2200} = 6.82 \text{ A}$
- Now,
 
$$\text{Regulation} = \frac{I_2(\text{FL}) \times (R_e'' \cos \Phi_2 \pm X_e'' \sin \Phi_2)}{V_{2\text{Rated}}} \times 100\%$$

$$\text{Regulation} = \frac{6.82 \times ((4.96 \times 0.8) \pm (17.07 \times 0.6))}{2200} \times 100\%$$

Regulation = +4.41% for lagging pf

Regulation = -1.94% for leading pf

# Thank You

Please contact the concerned teachers for any further doubts.