

# Meter Selection (MI)

DCT

$V_o \rightarrow 110V \rightarrow 0-150/300V$  ✓

$I_o \rightarrow 0.18A \rightarrow 0-1/2A$  ✓

$W_o \rightarrow$  Ratings Prim. Voltmeter + Primar Amm

$V_2 \rightarrow 220V \cdot 0-150/300V$  ✓

$W_o \rightarrow \left. \begin{matrix} 0-1/2A \\ 0-150/300V \end{matrix} \right\}$

SCT

$V_{sc} \rightarrow 22V \rightarrow 0-30/60V$  ✓

$I_{sc} \rightarrow 4.5A \rightarrow 0-5/10A$  ✓  
(0, -5A) ✓


$W_{sc} \rightarrow 0-30/60V$   
 $0-5/10A$

$I_2 \rightarrow 9A \rightarrow 0-10A/15A$

## Equivalent Ckt of 1 $\phi$ Transformer

①

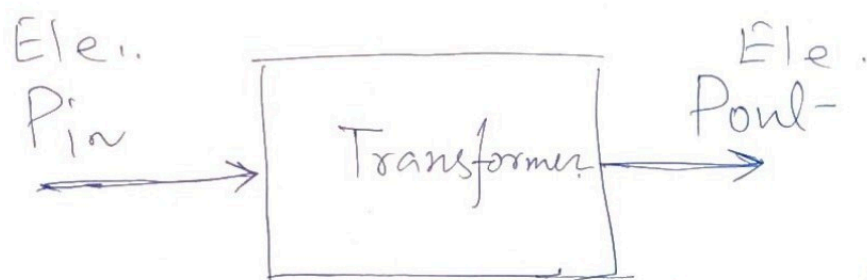1. 1 $\phi$  Transformers are the trans. which deal with single phase power.





by changing the levels of  $V$  and  $I$   
 $f$  will be fixed.

We need to  
increase  $V$   
or decrease  $V$  } Requirement of P.S.

# Faraday's EM Principle

②

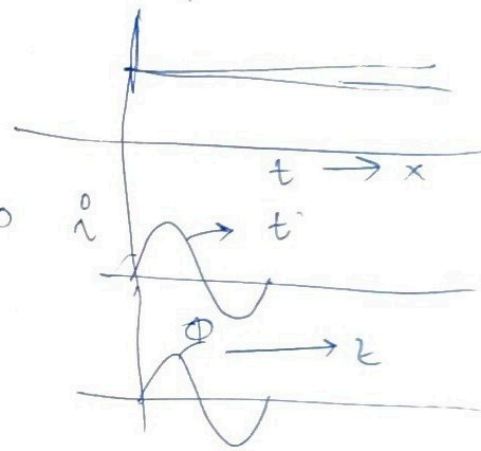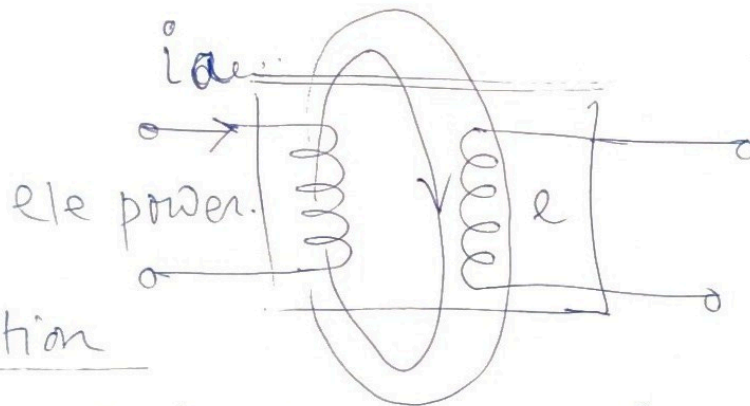

## Interaction

$\Phi$  and Conductor  $\rightarrow$  if we have relative motion either in time or in space.

$\downarrow \Phi = \Phi(t)$

$(e \propto \omega)$

$e = 444 \Phi_m f N$



$e_1 = 4.44 \Phi_m f N_1$

$e_2 = 4.44 \Phi_m f N_2$

③
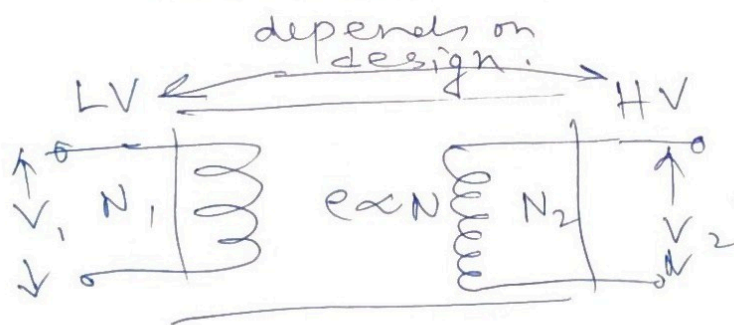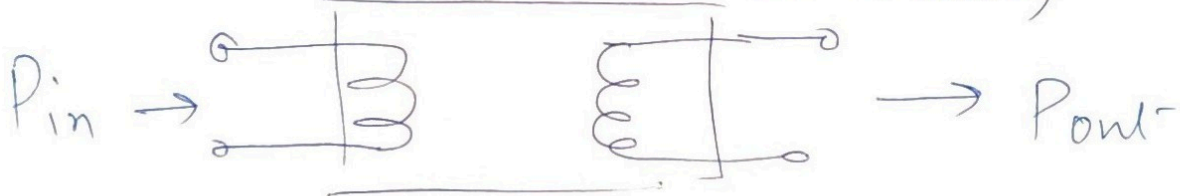
## Names of Windings

✓ Primary  $\xleftarrow{\text{depends on application}}$  Secondary ✓




$$N_2 > N_1 \Rightarrow V_2 > V_1$$
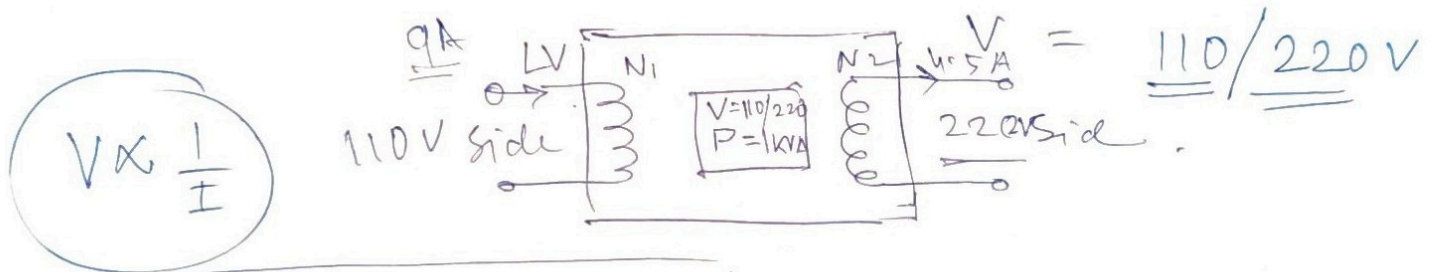
## Rating of Transformer

④

Rated Parameters.  $P = 1 \text{ kVA} = 10^3 \text{ VA}$



$$P = V_1 I_1 = V_2 I_2 \quad \left[ \because \cos \phi = 1 \right] 0.95$$

$$\frac{V_1}{110} I_1 = \frac{V_2}{220} I_2 = P_r = 10^3$$

$$I_{r1} = \frac{P_r}{V_{r1}} = \frac{10^3}{110} = 9.1 \text{ A} \rightarrow \text{Rated current of LV side}$$


$$I_{r2} = \frac{P_r}{V_{r2}} = \frac{10^3}{220} = 4.55 \text{ A} \rightarrow \text{Rated current of HV side}$$

## Equivalent Ckt of $1\phi$ Tr.

⑤



1. OCT

2. SC

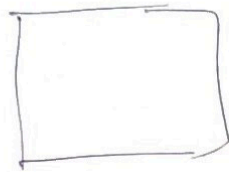

$\equiv$  combination of  
ele. ckt. elem.

$\rightarrow$  Equ. Ckt

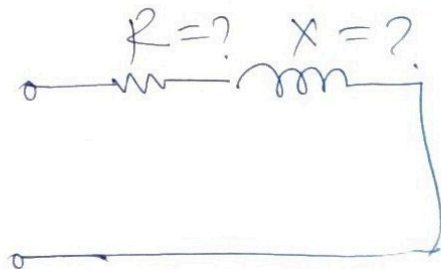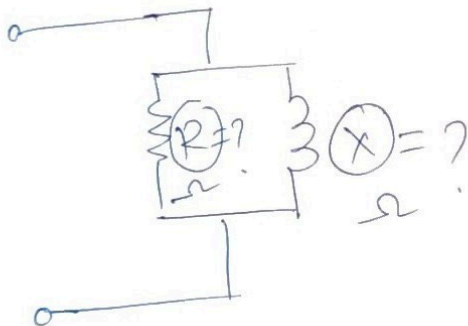




## OCT of 1 $\phi$ Tr.

(6)

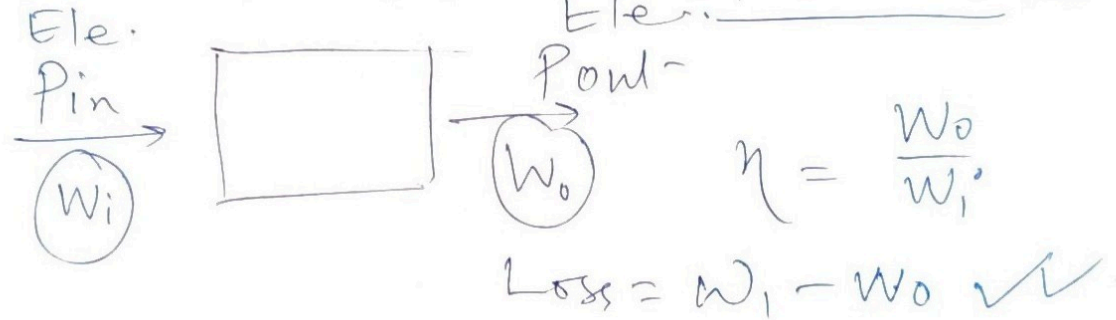1. To calculate the  $\eta$  ✓ Direct method,
2. To calculate the loss ✓ Ele. Direct method,




1.  $\eta$  ✓
2. L ✓  $\rightarrow$  We get I-loss C-loss separately
3. Equ. ckt parameters:  
OCT + SCT

(7)

## Trans Losses

performance of two materials.

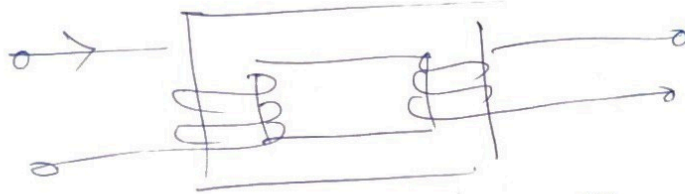


① Copper.

② Iron.

Copper  $\rightarrow$   $I$  flows  $\rightarrow$   $P_C L = I^2 R_1$   
 $SCL = I_2^2 R_2$

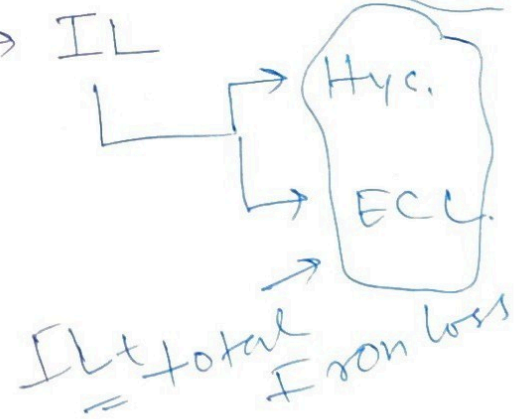Iron  $\rightarrow$   $\phi$  conducts  $\rightarrow$   $IL$






10  
220V  
50Hz  
AC

1. HV  $\rightarrow$  Secondary
2. HV  $\rightarrow$  Open.

⑧

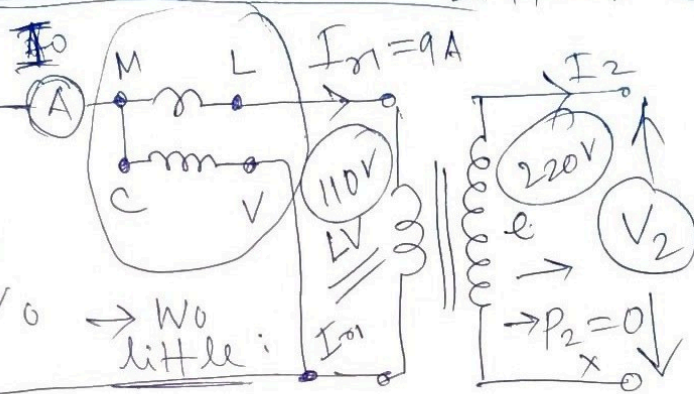

$Z_V = \infty$  very large.

open cell

$$\begin{aligned} \Gamma_2 &= 0 \\ \Gamma_2^2 \Gamma_2 &= 0 \end{aligned}$$

$$\underline{P_2 = V_2 I_2 = 0}$$

$W_0 = \underline{IL}_{\text{total key ckt}}$

$$P_1 = V_1 I_1 \quad \underline{P_2 =}$$

wass  $\underline{110} = I_1 = \text{wass.}$

$V_0$	$I_0$	$W_0^W$	$V_2$
25			
50			
75			
100			
110			220


2-5% of rated value.  
2% of 9A [ $\because I_{r1} = 9A$ ]

$$(\underline{0.18A})^2 R_1 \approx 0$$

$PCL = 0 \quad SCL = 0 \quad C_L = \begin{matrix} PCL \\ + \\ SCL \\ = 0 \end{matrix}$   
Completed

SCT of 10 Tr.

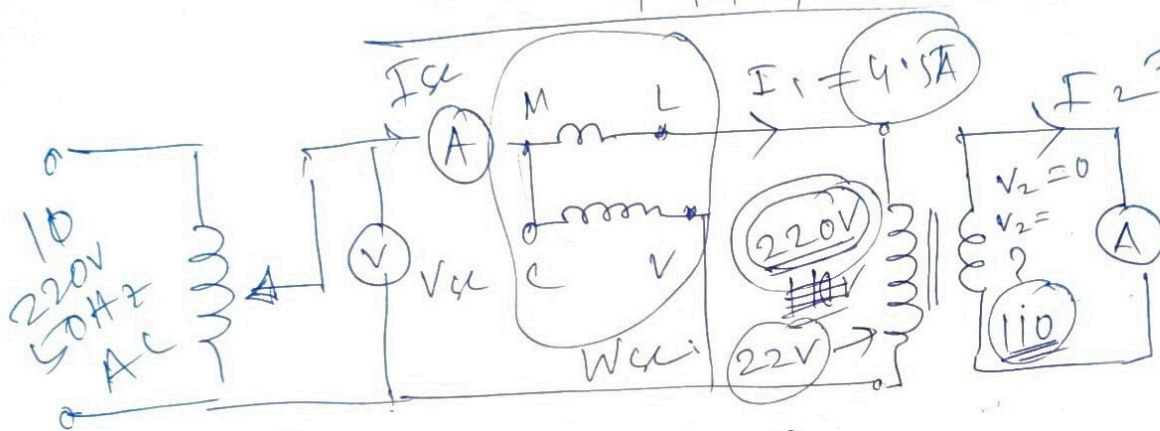1. LV side  $\rightarrow$  Secondary  
2. LV will be shorted



$$Z_2 \rightarrow 0$$

$$I_2 = \frac{110}{Z_2} \approx \text{HUGE}$$

Creating ~~loss~~ heat  
of huge amount  
 $\rightarrow$  will burn  
the tr.

10% of rated value (220V)

i.e. 22V will produce 9A at s.c.c.,  
and 4.5A at prim.

$W_x$  will be CL total.

$I_L \rightarrow$  depends on voltage  $\rightarrow$  SCT  $\rightarrow N_o \rightarrow I_L = 0$

Set Data

$V_{ce}$	$I_{ce}$	$W_{ce}$	$I_z$
			2A
			4A
			6A
			8A
			9A

22

## Meter Selection (MI)

OCT

$$V_o \rightarrow 110V \rightarrow \underline{0-150/300V} \checkmark$$

$$I_o \rightarrow 0.18A \rightarrow \underline{0-1/2A} \checkmark$$

$W_o \rightarrow$  Rating Prim. Voltmeter + Prim. Amm

$$V_2 \rightarrow \underline{220V} \cdot \underline{0-150/300V} \checkmark$$

$$W_o \rightarrow \left. \begin{array}{l} 0-1/2A \\ 0-150/300V \end{array} \right\}$$

SCT


$$V_{sc} \rightarrow 22V \rightarrow \underline{0-30/60V} \checkmark$$

$$I_{sc} \rightarrow 9.5A \rightarrow \underline{0-10A} \checkmark \quad (0.5A \checkmark)$$

$$W_{sc} \rightarrow \begin{array}{l} 0-30/60V \\ 0-5/10A \end{array}$$


$$I_2 \rightarrow 9A \rightarrow 0-10A/15A$$

# Connection Procedure.

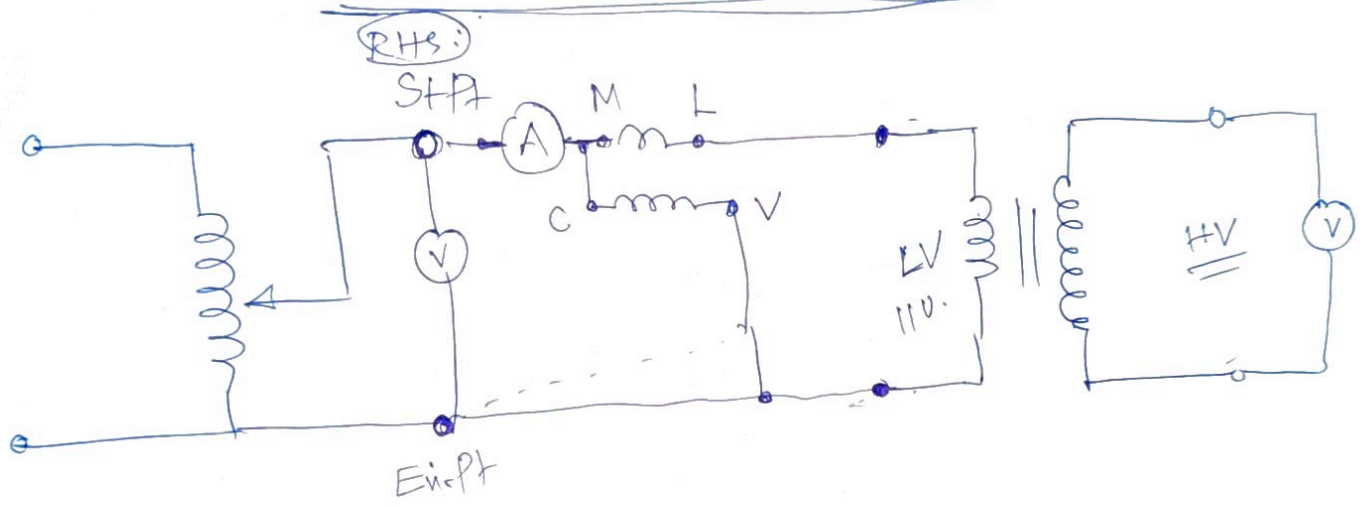

## Meter Reading

13

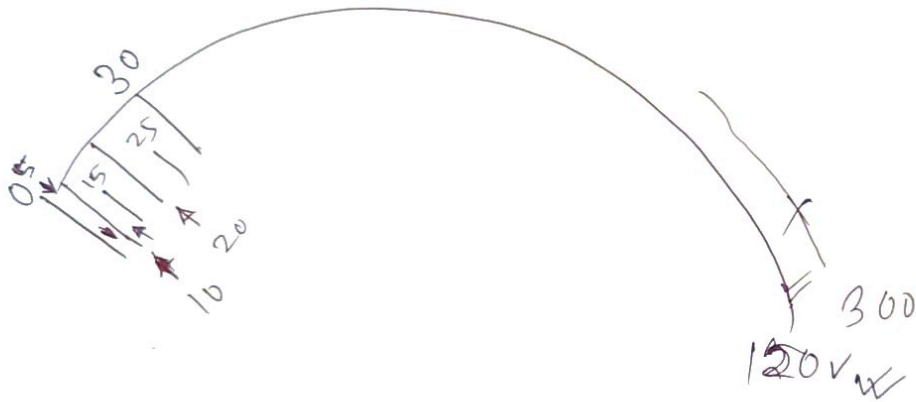



(14)


## Eqv. Ckt Parameter Calculation

OCT  $W_0 = V_0 I_0 \cos \phi_0$  ✓

$\sin \phi_0$  is known

$I_W = I_0 \cos \phi_0$

$I_M = I_0 \sin \phi_0$

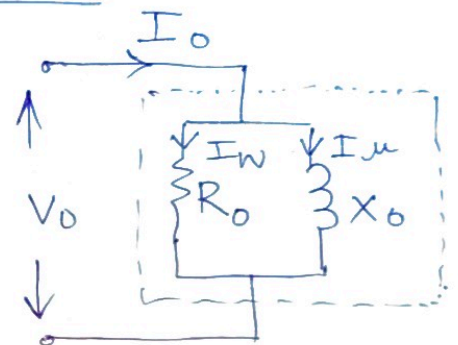



$R_0 = \frac{V_0}{I_W}$   $\because V_0 = I_W \cdot R_0$

$I_W = I_0 \cos \phi_0$   
 $I_M = I_0 \sin \phi_0$

$X_0 = \frac{V_0}{I_M}$   $\because V_0 = I_M X_0$

When  $X_0$  and  $R_0$  are known OCT Eq. ch is known

# SCT - Eq. Ckt

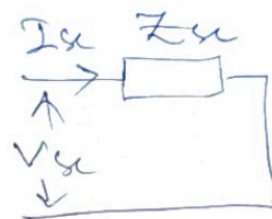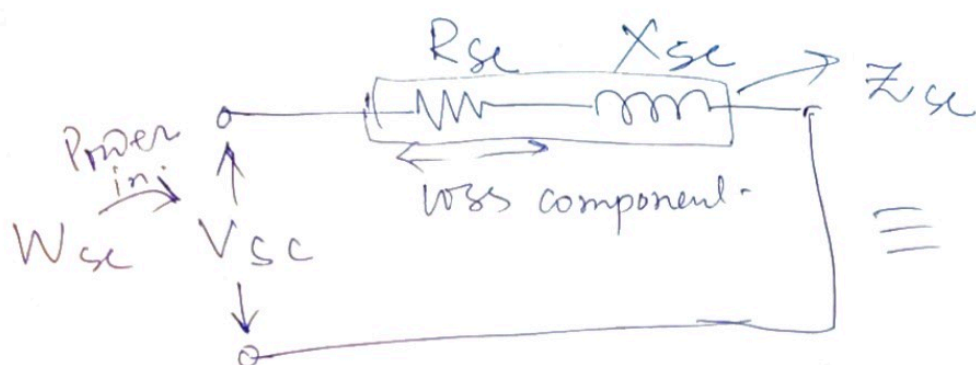

$$W_{sc} = I_{sc}^2 R_{sc}$$

Total impedance =  $Z_c$ , say,

$$Z_{sc} = R_{sc} + jX_{sc}$$

$$Z_{sc}^2 = R_{sc}^2 + X_{sc}^2$$

$$X_{sc} = \sqrt{Z_{sc}^2 - R_{sc}^2}$$

$$Z_{sc} = \frac{V_{sc}}{I_{sc}}$$

$R_{sc}$  and  $X_{sc}$  are obtained  
 SCT EC. is known.