
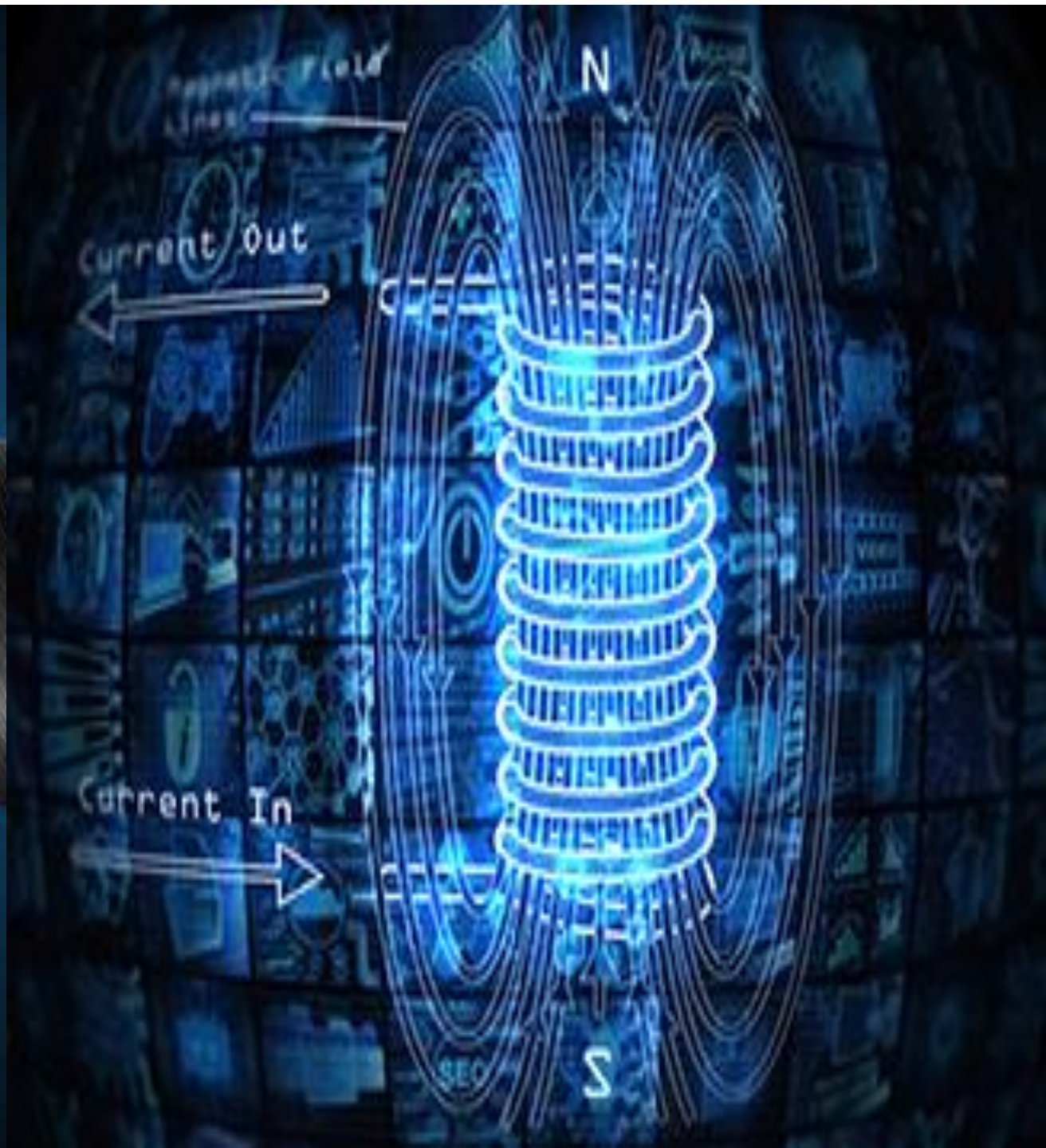


Electrical Engineering

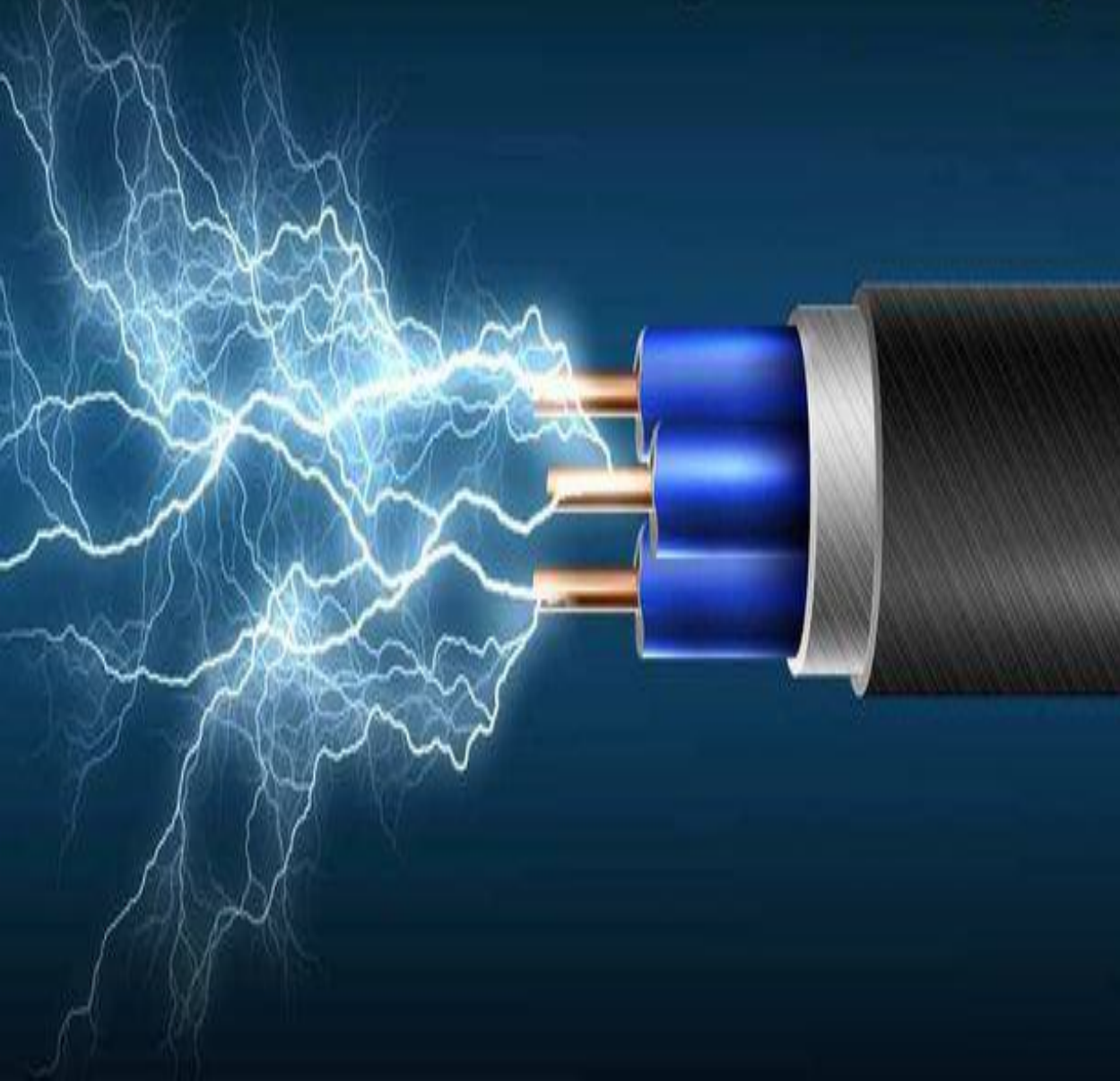

LECTURE 12

Transients

➤ **Steady State and Transient Response**

✓ **Steady State**

- A circuit having constant sources is said to be in steady state if the currents and voltages do not change with time.
- A circuit having sinusoidal currents and voltages of constant amplitude and constant frequency are also considered to be in a steady state.

✓ **Transient State**

- A circuit is said to be in transient state if the currents and voltages change from one steady state to another steady state.
- The behaviour of the voltage or current of the circuit containing energy storage elements is changed from one state to another with change in excitation.
- The time taken for the circuit to change from one state to other state is called the transient time.
- The application of KVL and KCL to circuits containing energy storage elements results in differential, rather than algebraic equations.

Transients

➤ **Steady State and Transient Response**

✓ **Transient State**

- The response of the circuit containing storage elements depends upon the nature of the circuit and so, it is called the natural response.
- Storage elements deliver their energy to the resistances. Hence the response change with time, gets saturated after some time, and is referred to as the transient response.
- When sources acting on a circuit, the response depends on the nature of the source or sources. This response is called forced response.

✓ **Complete Response**

- The complete response of a circuit consists of two parts: the forced response and the transient response.
- The complete solution consists of two parts: the complementary function and the particular solution.
- The complementary function dies out after short interval, and is referred to as the transient response or source free response.
- The particular solution is the steady state response, or the forced response.

Transients

✓ DC RESPONSE OF AN R-L CIRCUIT

Consider a circuit consisting of a resistance and inductance as shown in **Fig. 5.1**.

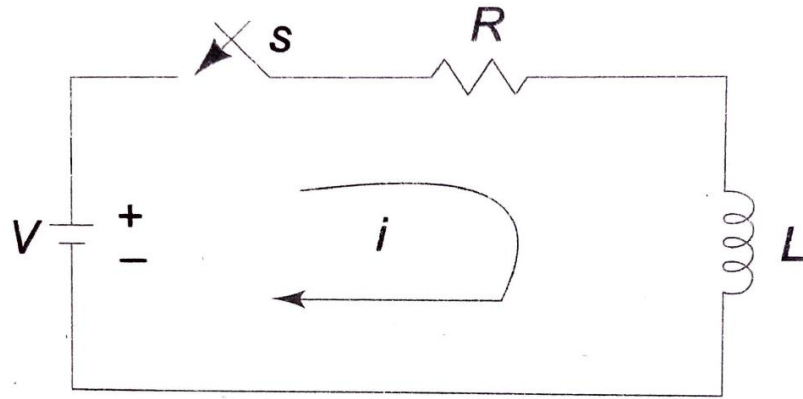


Fig. 5.1

The inductor in the circuit is initially uncharged and is in series with the resistor.

Now, the switch S is closed and the voltage V is applied to the circuit.

Apply Kirchhoff's Voltage Law to the circuit. We get the following differential equation.

$$V = Ri + L \frac{di}{dt}$$

$$\text{or } \frac{di}{dt} + \frac{R}{L}i = \frac{V}{L}$$

Where, V is the constant applied voltage and the current i is to be found out.

Transients

✓ DC RESPONSE OF AN R-L CIRCUIT

The equation is a linear differential equation of first order. Now, compare it with the following non-homogeneous differential equation

$$\frac{dx}{dt} + Px = K$$

Whose solution is

$$x = e^{-pt} \int K e^{+Pt} dt + c e^{-Pt} \quad \text{where, } c \text{ is an arbitrary constant.}$$

Similarly, the current equation is

$$i = c e^{-(R/L)t} + e^{-(R/L)t} \int \frac{R}{L} e^{(R/L)t} dt$$

$$\text{or, } i = c e^{-(R/L)t} + \frac{V}{R}$$

Transients

✓ DC RESPONSE OF AN R-L CIRCUIT

- **Determination of the value of c by using the initial conditions.**

In the circuit as shown in **Fig. 5.1**, the switch S is closed at $t = 0$.

At $t = 0^-$, i.e. just before closing the switch S , the current in the inductor is zero.

Since the inductor does not allow sudden changes in currents, at $t = 0^+$ just after the switch is closed, the current remains zero.

Thus at

$$t = 0, \quad i = 0$$

So,

$$0 = c + \frac{V}{R}$$

Hence

$$c = -\frac{V}{R}$$

Transients

✓ DC RESPONSE OF AN R-L CIRCUIT

$$\therefore i = \frac{V}{R} - \frac{V}{R} e^{-(R/L)t} = \frac{V}{R} [1 - e^{-(R/L)t}]$$

This equation consists of two parts, the steady state part V/R , and the transient part $(V/R)e^{-(R/L)t}$.

When switch S is closed, the response reaches a steady state value after a time interval as shown in **Fig. 5.2**

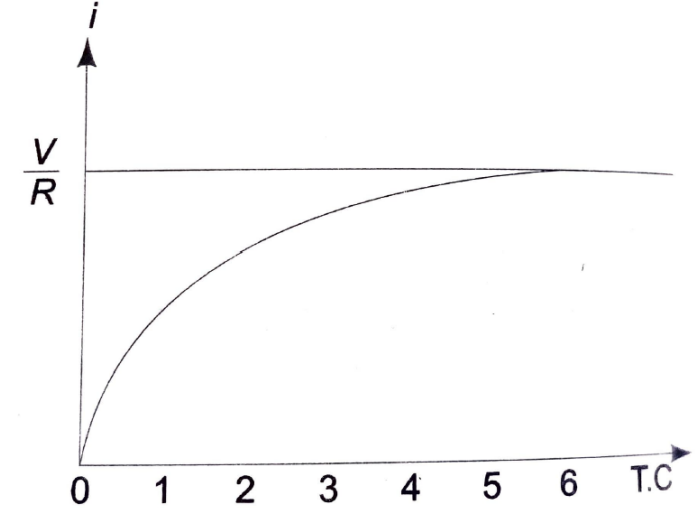


Fig. 5.2

Here the transition period is defined as the time taken for the current to reach its final or steady state value from its initial value.

The quantity L/R is important in describing the curve since L/R is the time required for the current to reach from its initial value of zero to the final value V/R .

The time constant of a function $\frac{V}{R} e^{-(R/L)t}$ is the time at which the exponent of e is unity, where e is the base of the natural logarithms. The term L/R is called the time constant and is denoted by τ

$$\therefore \tau = \frac{L}{R} \text{ sec}$$

Transients

✓ DC RESPONSE OF AN R-L CIRCUIT

∴ The transient part of the solution is

$$i = \frac{V}{R} e^{-(R/L)t} = \frac{V}{R} e^{-\frac{t}{\tau}}$$

At one TC, i.e. at one time constant, the transient term reaches 36.8 percent of its initial value.

$$i(\tau) = -\frac{V}{R} e^{-\frac{t}{\tau}} = -\frac{V}{R} e^{-1} = -0.368 \frac{V}{R}$$

Similarly,

$$i(2\tau) = -\frac{V}{R} e^{-2} = -0.135 \frac{V}{R}$$

$$i(3\tau) = -\frac{V}{R} e^{-3} = -0.0498 \frac{V}{R}$$

$$i(5\tau) = -\frac{V}{R} e^{-5} = -0.0067 \frac{V}{R}$$

After 5 TC, the transient part reaches more than 99 percent of its initial value.

Transients

✓ DC RESPONSE OF AN R-L CIRCUIT

Voltage across the resistor is

$$v_R = Ri = R \times \frac{V}{R} [1 - e^{-(R/L)t}] = V[1 - e^{-(R/L)t}]$$

Similarly, the voltage across the inductance is

$$v_L = L \frac{di}{dt} = L \times \frac{V}{R} \times \frac{R}{L} e^{-(R/L)t} = V e^{-(R/L)t}$$

The response are shown in **Fig. 5.3**

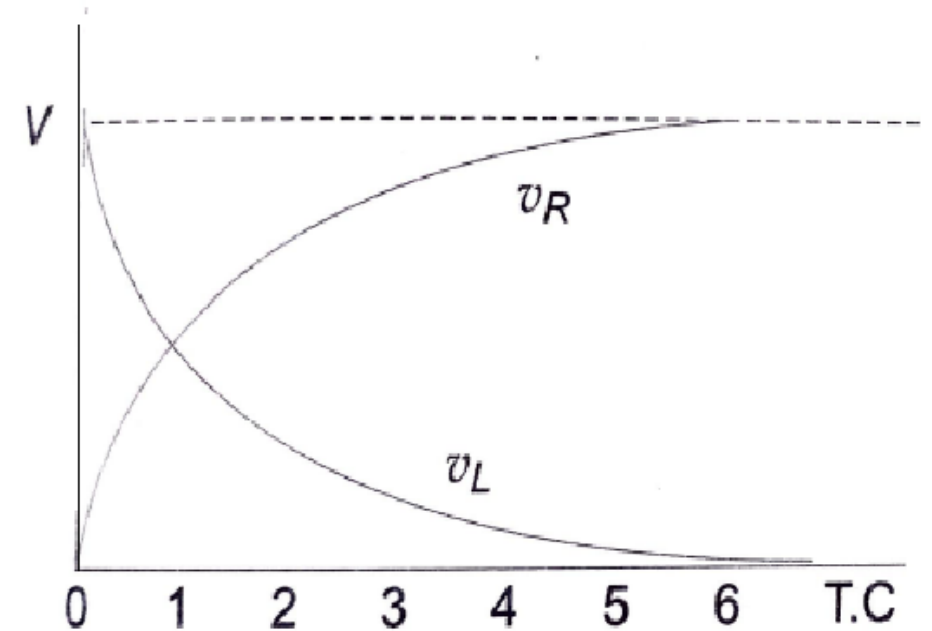


Fig. 5.3

Transients

✓ DC RESPONSE OF AN R-L CIRCUIT

Power in the resistor is

$$P_R = v_R i = V[1 - e^{-(R/L)t}] \times \frac{V}{R}[1 - e^{-(R/L)t}]$$

$$\therefore P_R = \frac{V^2}{R} [1 - 2e^{-(R/L)t} + e^{-(2R/L)t}]$$

Power in the inductor is

$$P_L = v_L i = V e^{-(R/L)t} \times \frac{V}{R} [1 - e^{-(R/L)t}]$$

$$\therefore P_L = \frac{V^2}{R} [e^{-(R/L)t} - e^{-(2R/L)t}]$$

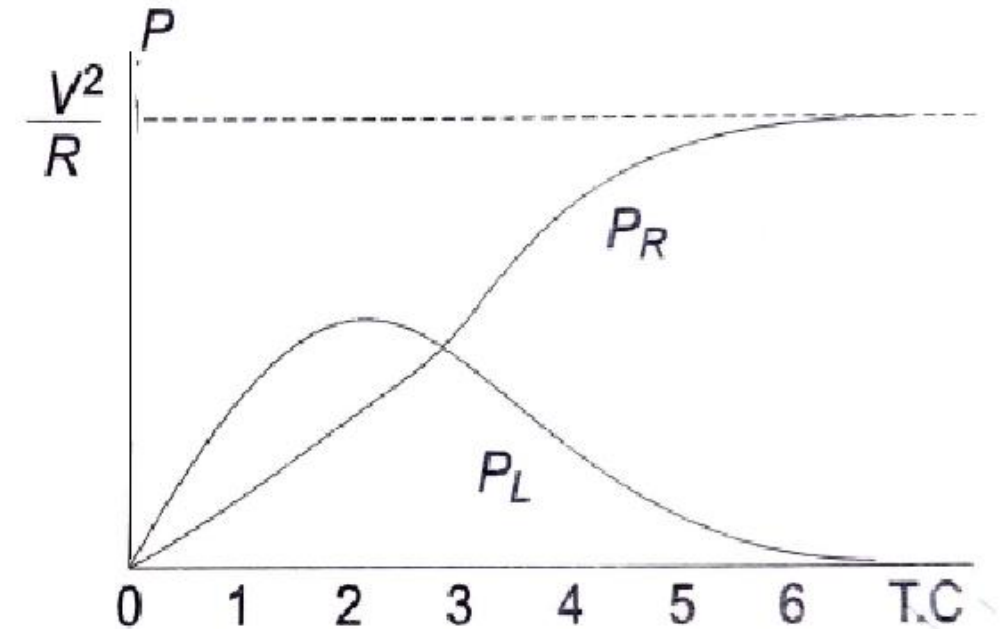


Fig. 5.4

The responses are shown in **Fig. 5.4**

Transients

Example – P5.1

A series RL circuit with $R = 30\ \Omega$ and $L = 15\ \text{H}$ has a constant voltage $V = 60\ \text{volt}$ applied at $t = 0$ as shown in **Fig. P5.1**. Determine the current

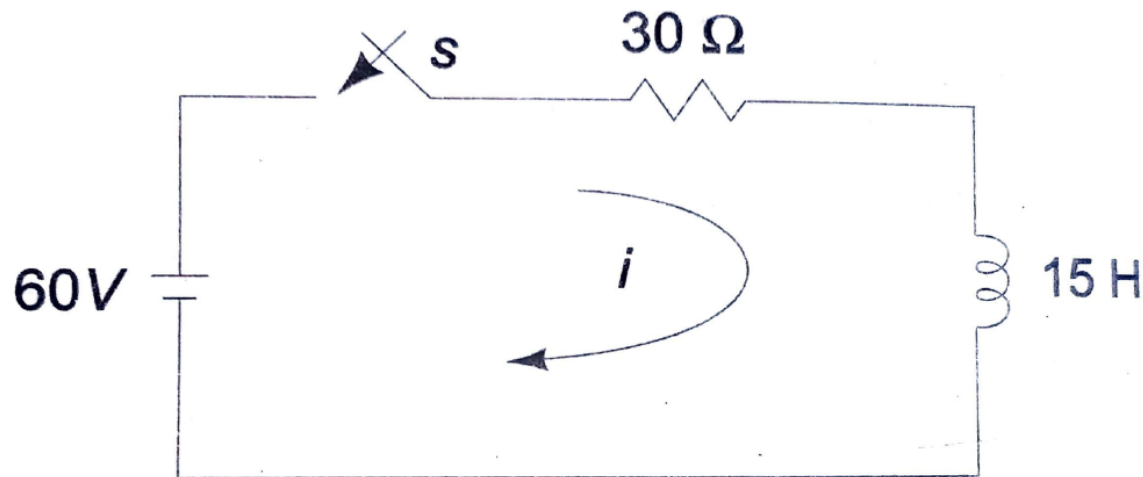


Fig. P5.1

Transients

Solution of Example – P5.1

By applying Kirchhoff's voltage law, we get

$$15 \frac{di}{dt} + 30i = 60$$

$$\therefore \frac{di}{dt} + 2i = 4$$

The general solution for a linear differential equation is

$$i = ce^{-Pt} + e^{-Pt} \int Ke^{Pt} dt$$

Where $P = 2, K = 4$

$$\therefore i = ce^{-2t} + e^{-2t} \int 4e^{2t} dt$$

$$\therefore i = ce^{-2t} + 2$$

Transients

Solution of Example – P5.1

At $t = 0$, the switch S is closed.

Since the inductor never allows sudden changes in currents. At $t = 0^+$ the current in the circuit is zero.

Therefore at $t = 0^+$, $i = 0$

$$\therefore 0 = c + 2 \qquad \therefore c = -2$$

Substituting the value of c in the current equation, we have

$$i = 2[1 - e^{-2t}] \text{ A}$$

Voltage across resistor

$$v_R = Ri = 30 \times 2[1 - e^{-2t}] = 60[1 - e^{-2t}]$$

Voltage across inductor

$$v_L = L \frac{di}{dt} = 15 \times \frac{d}{dt} [2(1 - e^{-2t})] = 30 \times 2e^{-2t} = 60e^{-2t} \text{ V}$$

Transients

➤ DC RESPONSE OF AN R-C CIRCUIT

Consider a circuit consisting of resistance and capacitance as shown in **Fig. 5.5**.

The capacitor in the circuit is initially uncharged and is in series with a resistor. The switch S is closed at $t = 0$ and the voltage V is applied to the circuit.

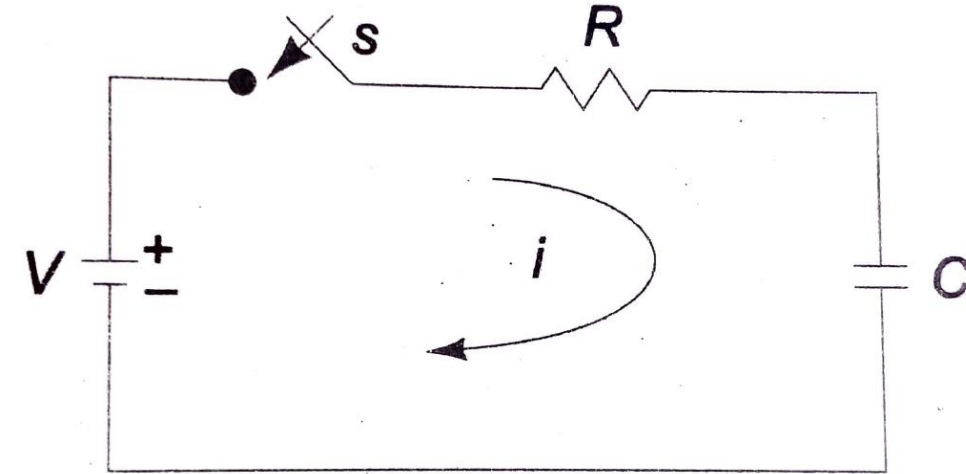


Fig. 5.5

Application of the Kirchhoff's voltage law to the circuit results in the following differential equation.

$$V = Ri + \frac{1}{C} \int i \, dt$$

By differentiating the above equation, we get

$$R \frac{di}{dt} + \frac{1}{C} i = 0$$

$$\text{or, } \frac{di}{dt} + \frac{1}{RC} i = 0$$

Transients

➤ DC RESPONSE OF AN R-C CIRCUIT

The equation is a linear differential equation with only the complementary function. The particular solution for the equation is zero.

The solution for this type of differential equation is $i = ce^{-(1/RC)t}$

Determination of the value of c by using the initial conditions.

In the circuit shown in **Fig. 5.5**, switch S is closed at $t = 0$.

Since the capacitor never allows sudden changes in voltage, it will act as a short circuit at $t = 0^+$.

So, the current in the circuit at $t = 0^+$ is V/R

At $t = 0$, the current $i = V/R$ $\therefore \frac{V}{R} = c$

So, the current equation becomes $i = \frac{V}{R} e^{-(1/RC)t}$

When switch S is closed, the response decays with time as shown in **Fig. 5.6**.

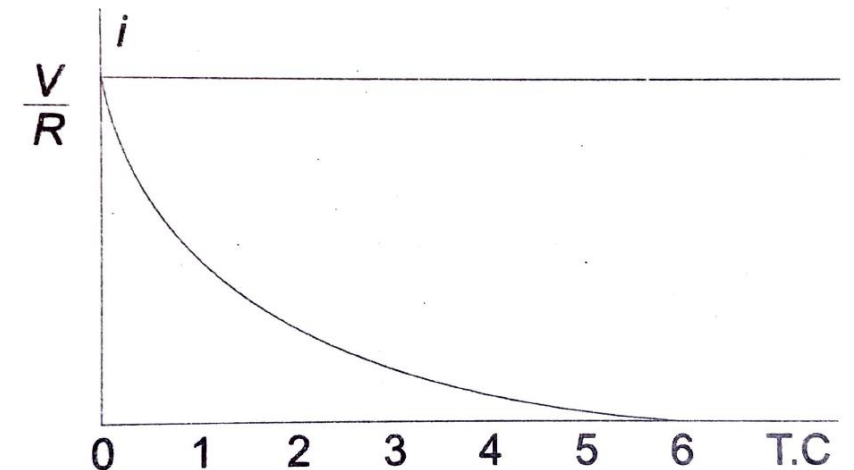


Fig. 5.6.

In the solution, the quantity RC is the time constant, and is denoted by τ , where $\tau = RC$ sec

After 5 TC, the curve reaches 99 per cent of its final value.

Transients

➤ DC RESPONSE OF AN R-C CIRCUIT

Voltage across the resistor

$$v_R = Ri = R \times \frac{V}{R} e^{-(1/RC)t} = V e^{-(1/RC)t}$$

Similarly, voltage across the capacitor

$$\begin{aligned} v_C &= \frac{1}{C} \int i \, dt = \frac{1}{C} \int \frac{V}{R} e^{-(1/RC)t} \, dt \\ &= - \left[\frac{V}{RC} \times RC e^{-(1/RC)t} \right] + c \\ &= -V e^{-(1/RC)t} + c \end{aligned}$$

At $t = 0$, voltage across capacitor is zero $\therefore c = V$

$$\therefore v_C = V[1 - e^{-(1/RC)t}]$$

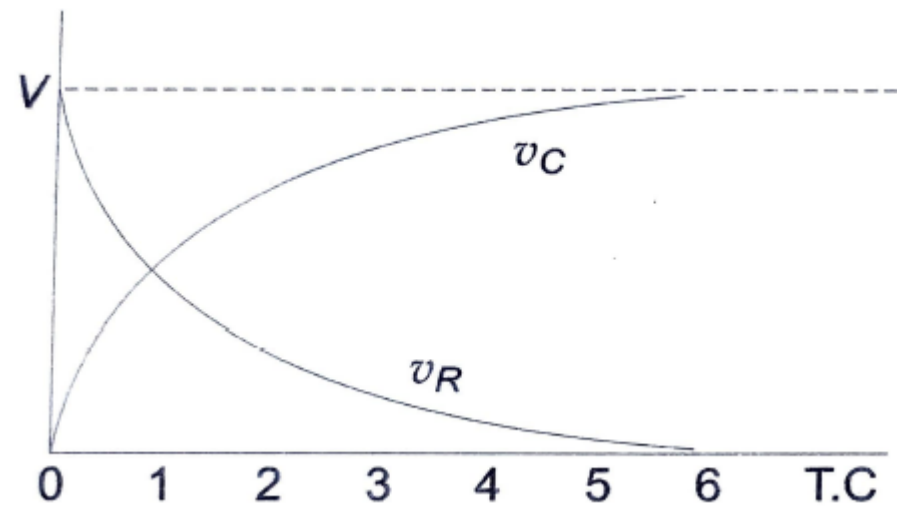


Fig. 5.7

The voltage across each element is shown in **Fig. 5.7**

Transients

➤ DC RESPONSE OF AN R-C CIRCUIT

Power in the resistor $P_R = v_R i = V e^{-(1/RC)t} \times \frac{V}{R} e^{-(1/RC)t} = \frac{V^2}{R} e^{-(2/RC)t}$

Power in the capacitor $P_C = v_C i = V [1 - e^{-(1/RC)t}] \times \frac{V}{R} e^{-(1/RC)t}$
 $= \frac{V^2}{R} [e^{-(1/RC)t} - e^{-(2/RC)t}]$

The responses are shown in **Fig. 5.8**

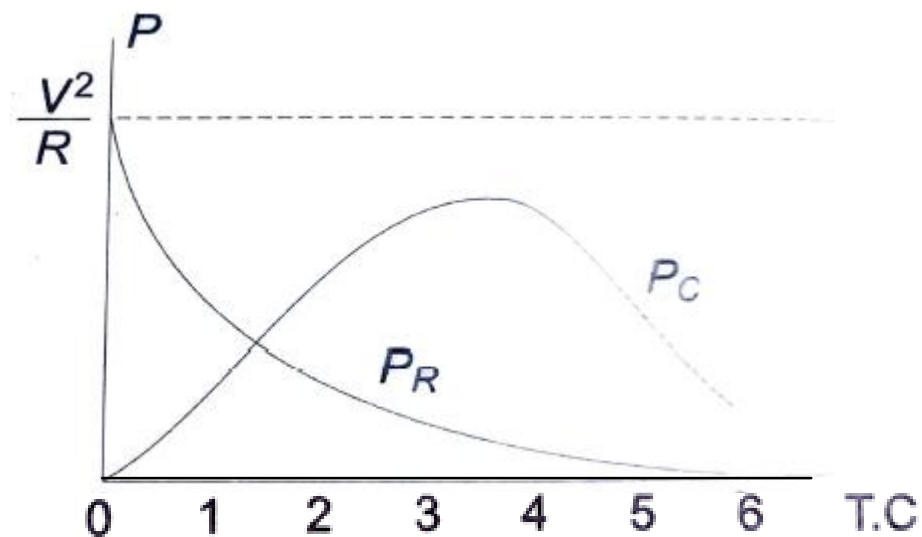


Fig. 5.8

Transients

Example – P5.2

A series RC circuit consists of resistor of $10\ \Omega$ and capacitor of $0.1\ \text{F}$ as shown in **Fig. P5.2**. A constant voltage of $20\ \text{V}$ is applied to the circuit at $t = 0$. Obtain the current equation. Determine the voltage across the resistor and the capacitor.

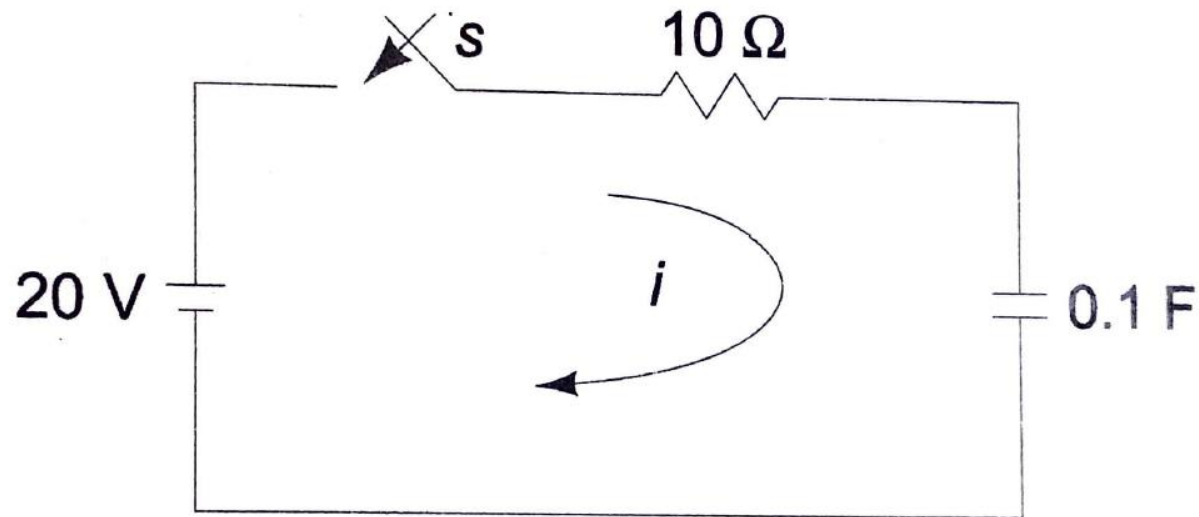


Fig. P5.2.

Transients

Solution of Example – P5.2

By applying Kirchhoff's law, we get

$$10i + \frac{1}{0.1} \int i dt = 20$$

Differentiating with respect to t we get

$$10 \frac{di}{dt} + \frac{i}{0.1} = 0$$
$$\therefore \frac{di}{dt} + i = 0$$

The solution for the above equation is $i = ce^{-t}$

At $t = 0$, switch S is closed. Since the capacitor does not allow sudden changes in voltage, the current in the circuit is $i = V/R = 20/10 = 2 \text{ A}$.

At $t = 0$, $i = 2 \text{ A}$

\therefore The current equation $i = 2e^{-t}$

Voltage across the resistor is $v_R = i \times R = 2e^{-t} \times 10 = 20e^{-t} \text{ V}$

Voltage across the capacitor is $v_C = V[1 - e^{-(1/RC)t}] = 20[1 - e^{-t}] \text{ V}$

Transients

➤ DC RESPONSE OF R-L-C CIRCUIT

Consider a circuit consisting of resistance, inductance and capacitance as shown in **Fig. 5.9**.

The capacitor and inductor are initially uncharged, and are in series with a resistor.

The switch S is closed at $t = 0$, and determine the complete solution for the current.

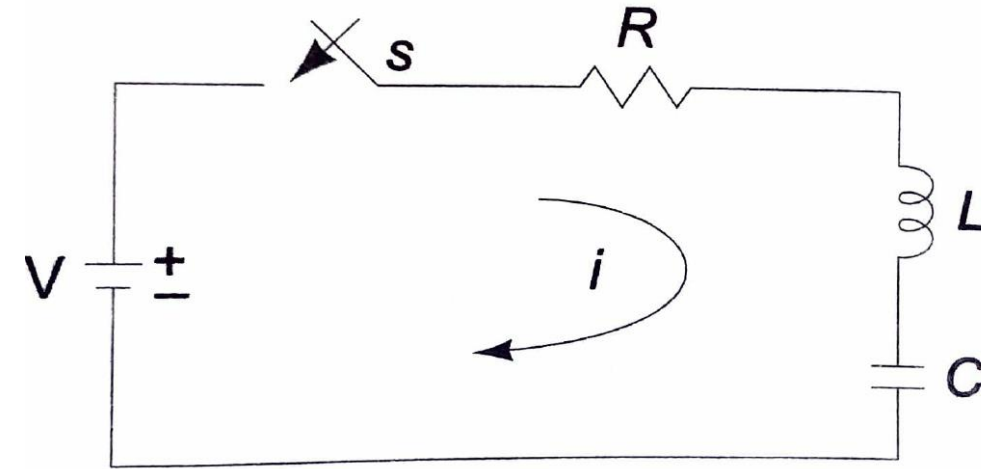


Fig. 5.9

Application of Kirchhoff's voltage law to the circuit results in the following differential equation.

$$V = Ri + L \frac{di}{dt} + \frac{1}{C} \int i dt$$

By differentiating the above equation, we have

$$0 = R \frac{di}{dt} + L \frac{d^2i}{dt^2} + \frac{1}{C} i$$

$$\text{or, } \frac{d^2i}{dt^2} + \frac{R}{L} \frac{di}{dt} + \frac{1}{LC} i = 0$$

Transients

➤ DC RESPONSE OF R-L-C CIRCUIT

The equation is a second order linear differential equation, with only complementary function. The particular solution for the equation is zero.

Characteristic equation for the above differential equation $\left(D^2 + \frac{R}{L}D + \frac{1}{LC}\right) = 0$

The roots of the equation are $D_1, D_2 = -\frac{R}{2L} \pm \sqrt{\left(\frac{R}{2L}\right)^2 - \frac{1}{LC}}$

By assuming $K_1 = -\frac{R}{2L}$ and $K_2 = \sqrt{\left(\frac{R}{2L}\right)^2 - \frac{1}{LC}}$

$\therefore D_1 = K_1 + K_2$ and $D_2 = K_1 - K_2$

Now, the current of R-L-C circuit for different cases are determined as follows:

Transients

➤ DC RESPONSE OF R-L-C CIRCUIT

Case 1: When $R = 0$

The roots are complex conjugate, thus the characteristic equation is written as

$$[D - jK_2][D + jK_2]i = 0$$


The solution for the equation is

$$\begin{aligned} i &= c_1 e^{(jK_2)t} + c_2 e^{(-jK_2)t} \\ &= c_1 e^{jK_2 t} + c_2 e^{-jK_2 t} \\ &= c_1 (\cos K_2 t + j \sin K_2 t) + c_2 (\cos K_2 t - j \sin K_2 t) \\ &= (c_1 + c_2) \cos K_2 t + j(c_1 - c_2) \sin K_2 t \\ &= A \cos K_2 t + B \sin K_2 t \quad [\because A = c_1 + c_2, \quad B = c_1 - c_2] \\ &= I_m \sin(K_2 t + \phi) \quad [\because I_m = \sqrt{A^2 + B^2}, \quad \phi = \tan^{-1}(A/B)] \end{aligned}$$

Transients

➤ DC RESPONSE OF R-L-C CIRCUIT

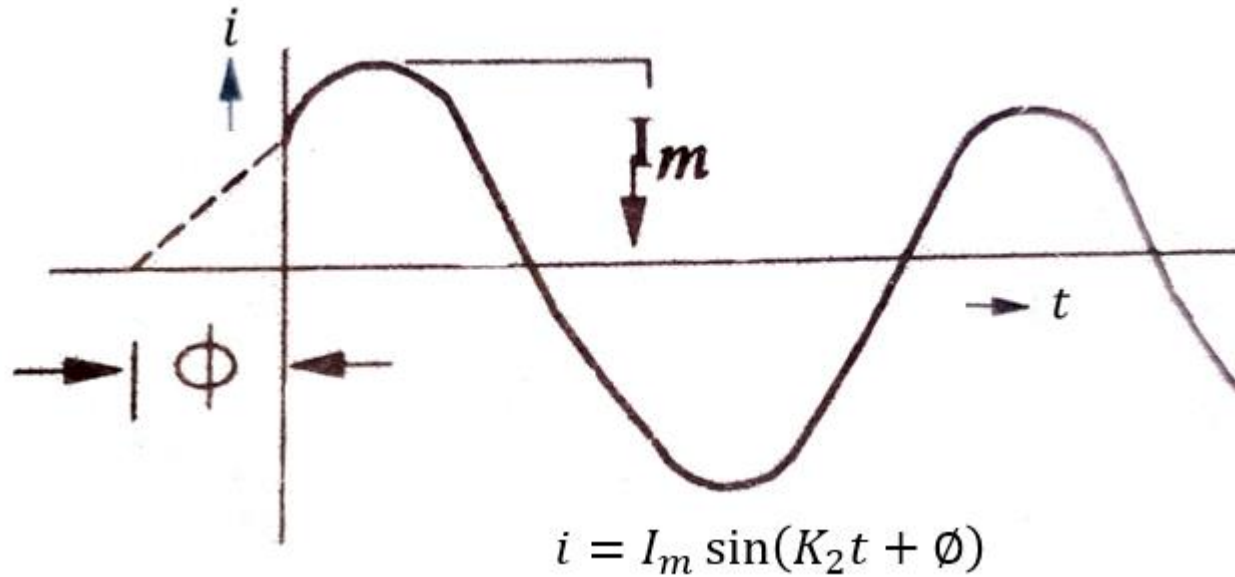The current, i as shown in **Fig. 5.10** is **undamped** in nature.



$$f = \frac{1}{2\pi} \sqrt{\frac{1}{LC}}$$

Fig. 5.10: Undamped Current Waveform

Transients

➤ DC RESPONSE OF R-L-C CIRCUIT

Case 2: when $\left(\frac{R}{2L}\right)^2 > \frac{1}{LC}$

The roots are real and unequal. So, the characteristic equation is written as

$$[D - (K_1 + K_2)][D - (K_1 - K_2)]i = 0$$

The solution for the above equation is

$$\begin{aligned} i &= c_1 e^{(K_1 + K_2)t} + c_2 e^{(K_1 - K_2)t} \\ &= e^{K_1 t} (c_1 e^{K_2 t} + c_2 e^{-K_2 t}) \\ &= e^{K_1 t} [c_1 (\cosh K_2 t + \sinh K_2 t) + c_2 (\cosh K_2 t - \sinh K_2 t)] \\ &= e^{K_1 t} [(c_1 + c_2) \cosh K_2 t + (c_1 - c_2) \sinh K_2 t] \\ &= e^{K_1 t} [A \cosh K_2 t + B \sinh K_2 t] \quad [\because A = c_1 + c_2, \quad B = c_1 - c_2] \end{aligned}$$

Transients

➤ DC RESPONSE OF R-L-C CIRCUIT

The current, i as shown in **Fig. 5.11** is **overdamped** in nature.

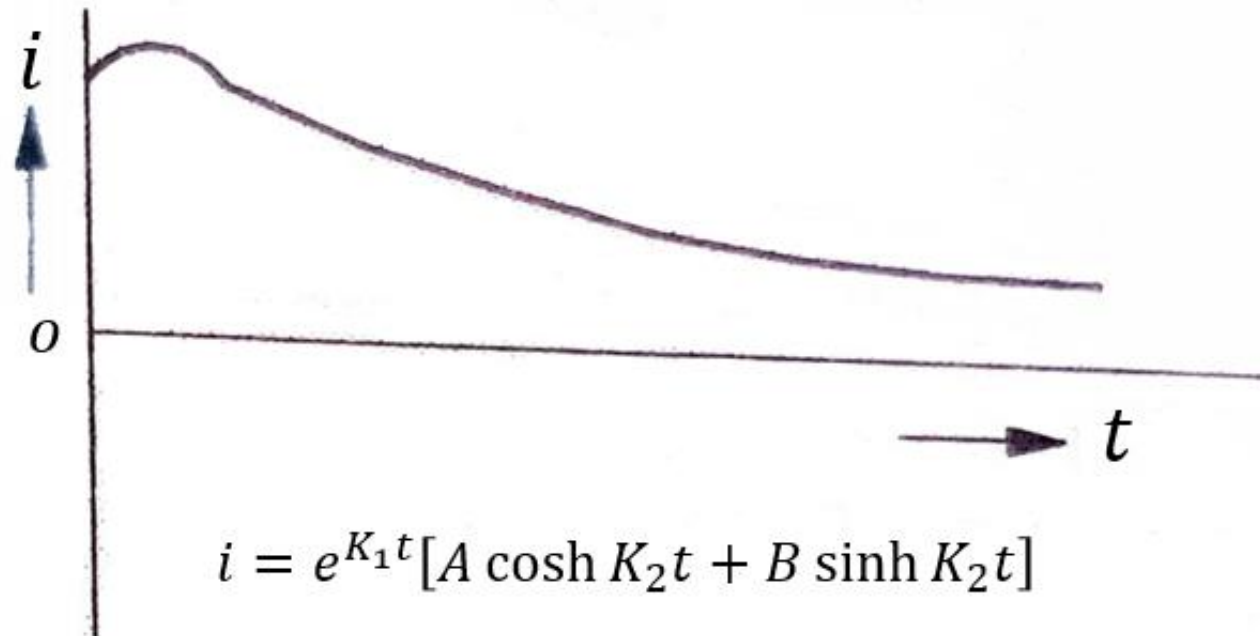


Fig. 5.11: Overdamped Current Waveform

Transients

➤ DC RESPONSE OF R-L-C CIRCUIT

Case 3: when $\left(\frac{R}{2L}\right)^2 < \frac{1}{LC}$

The roots are complex conjugate, thus the characteristic equation is written as

$$[D - (K_1 + jK_2)][D - (K_1 - jK_2)]i = 0$$

The solution for the above equation is

$$i = c_1 e^{(K_1 + jK_2)t} + c_2 e^{(K_1 - jK_2)t}$$

$$= e^{K_1 t} (c_1 e^{jK_2 t} + c_2 e^{-jK_2 t})$$

$$= e^{K_1 t} [c_1 (\cos K_2 t + j \sin K_2 t) + c_2 (\cos K_2 t - j \sin K_2 t)]$$

$$= e^{K_1 t} [(c_1 + c_2) \cos K_2 t + j(c_1 - c_2) \sin K_2 t]$$

$$= e^{K_1 t} [A \cos K_2 t + B \sin K_2 t] \quad [\because A = c_1 + c_2, \quad B = c_1 - c_2]$$

$$i = I_m e^{K_1 t} \sin(K_2 t + \phi) \quad \left[\because I_m = \sqrt{A^2 + B^2}, \quad \phi = \tan^{-1}(A/B) \right] \quad 25$$

Transients

➤ DC RESPONSE OF R-L-C CIRCUIT

The current, i as shown in **Fig. 5.12** is **underdamped** in nature.

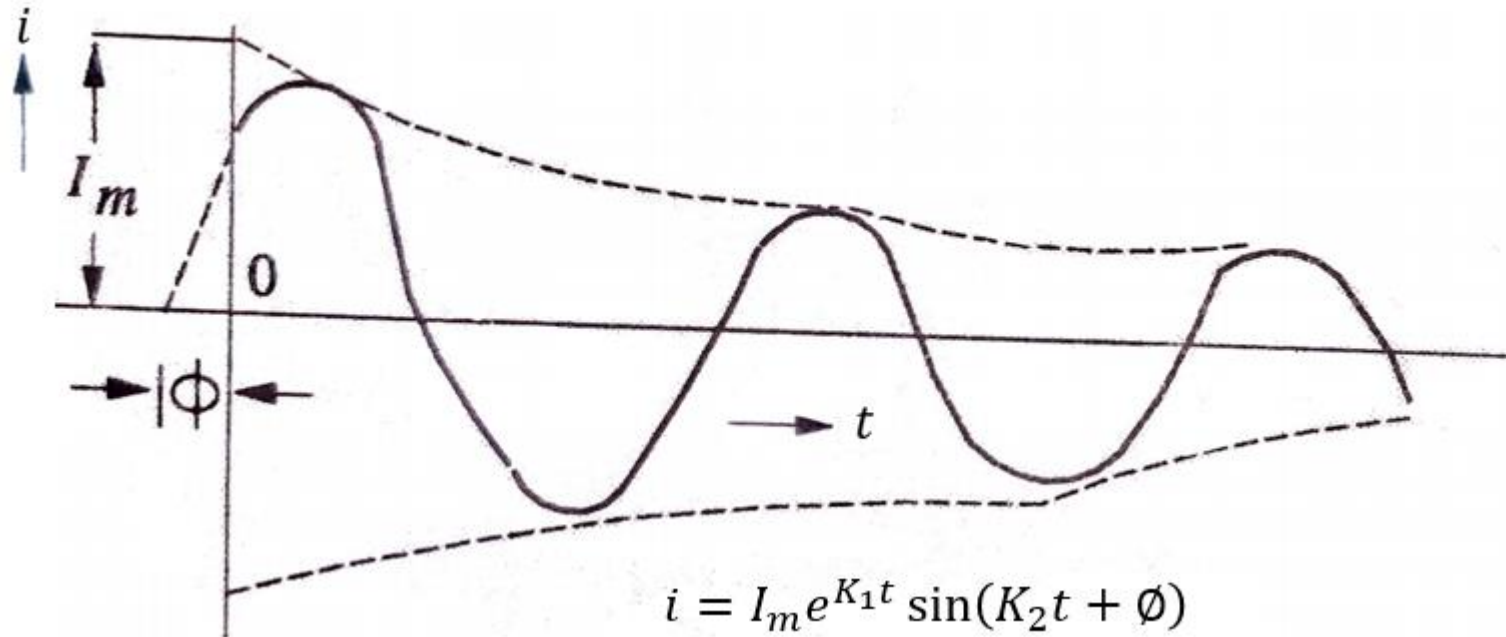


Fig. 5.12: Underdamped Current Waveform

$$\therefore f = \frac{1}{2\pi} \sqrt{\left(\frac{R}{2L}\right)^2 - \frac{1}{LC}}$$

= Natural frequency
of the circuit.

Transients

➤ DC RESPONSE OF R-L-C CIRCUIT

Case 4: when $\left(\frac{R}{2L}\right)^2 = \frac{1}{LC}$

The roots are equal, and thus the characteristic equation is written as

$$(D - K_1)(D - K_1)i = 0$$

The solution for the equation is

$$i = e^{K_1 t}(c_1 + c_2 t)$$

The current, i as shown in **Fig. 5.13** is **critically damped** in nature.

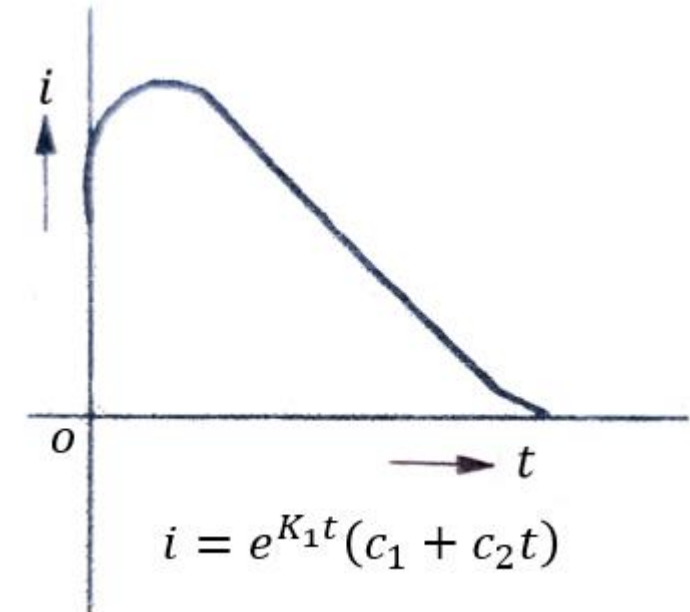


Fig. 5.13: Critically Damped Current Waveform

Transients

Example – P5.3

The circuit shown in **Fig. P5.3** consists of resistance, inductance and capacitance in series with a 100 V constant source when the switch is closed at $t = 0$. Find the current transient.

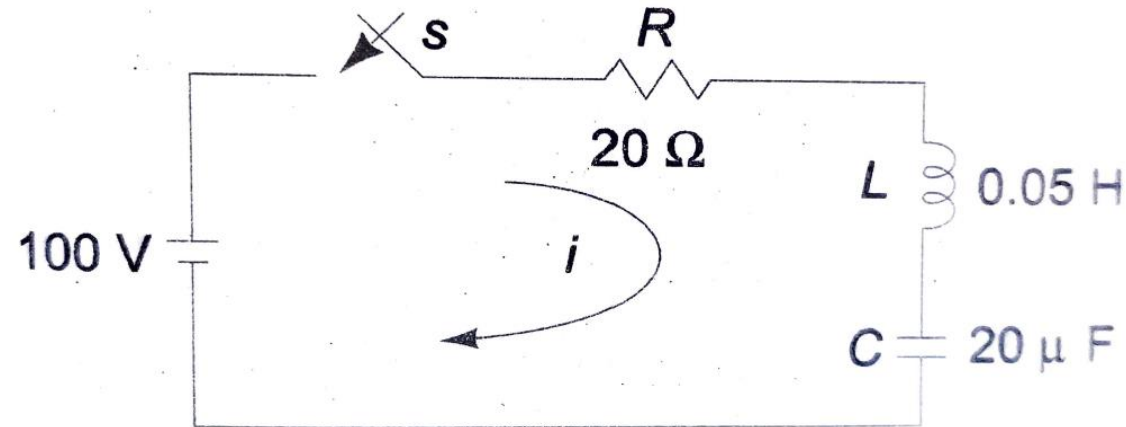


Fig. P5.3

Transients

Solution of Example – P5.3

At $t = 0$, switch S is closed when the 100 V source is applied to the circuit and results in the following differential equation.

$$100 = 20i + 0.05 \frac{di}{dt} + \frac{1}{20 \times 10^{-6}} \int i dt$$

Differentiating, we get

$$0.05 \frac{d^2 i}{dt^2} + 20 \frac{di}{dt} + \frac{1}{20 \times 10^{-6}} i = 0$$

$$\frac{d^2 i}{dt^2} + 400 \frac{di}{dt} + 10^6 i = 0$$

$$(D^2 + 400D + 10^6)i = 0$$

$$D_1, D_2 = -\frac{400}{2} \pm \sqrt{\left(\frac{400}{2}\right)^2 - 10^6}$$

$$= -200 \pm \sqrt{(200)^2 - 10^6}$$

$$D_1 = -200 + j979.8$$

$$D_2 = -200 - j979.8$$

Therefore the current

$$i = e^{+K_1 t} [c_1 \cos K_2 t + c_2 \sin K_2 t]$$

Transients

Solution of Example – P5.3

At $t = 0$, the current flowing through the circuit is zero

$$i = 0 = (1)[c_1 \cos 0 + c_2 \sin 0] \quad \therefore c_1 = 0$$

$$\therefore i = e^{-200t} c_2 \sin 979.8t \text{ A}$$

Differentiating, we get $\frac{di}{dt} = c_2[e^{-200t} 979.8 \cos 979.8t + e^{-200t} \sin 979.8t]$

At $t = 0$, the voltage across inductor is 100 V

$$\therefore L \frac{di}{dt} = 100 \quad \text{or,} \quad \frac{di}{dt} = 2000$$

$$\text{At } t = 0 \quad \frac{di}{dt} = 2000 = c_2 979.8 \cos 0$$

$$\therefore c_2 = \frac{2000}{979.8} = 2.04$$

The current equation is $i = e^{-200t} (2.04 \sin 979.8t) \text{ A}$



Thank you