

ECC-01


Module 3: Diode Circuits

Diode Circuits [3 Hours]

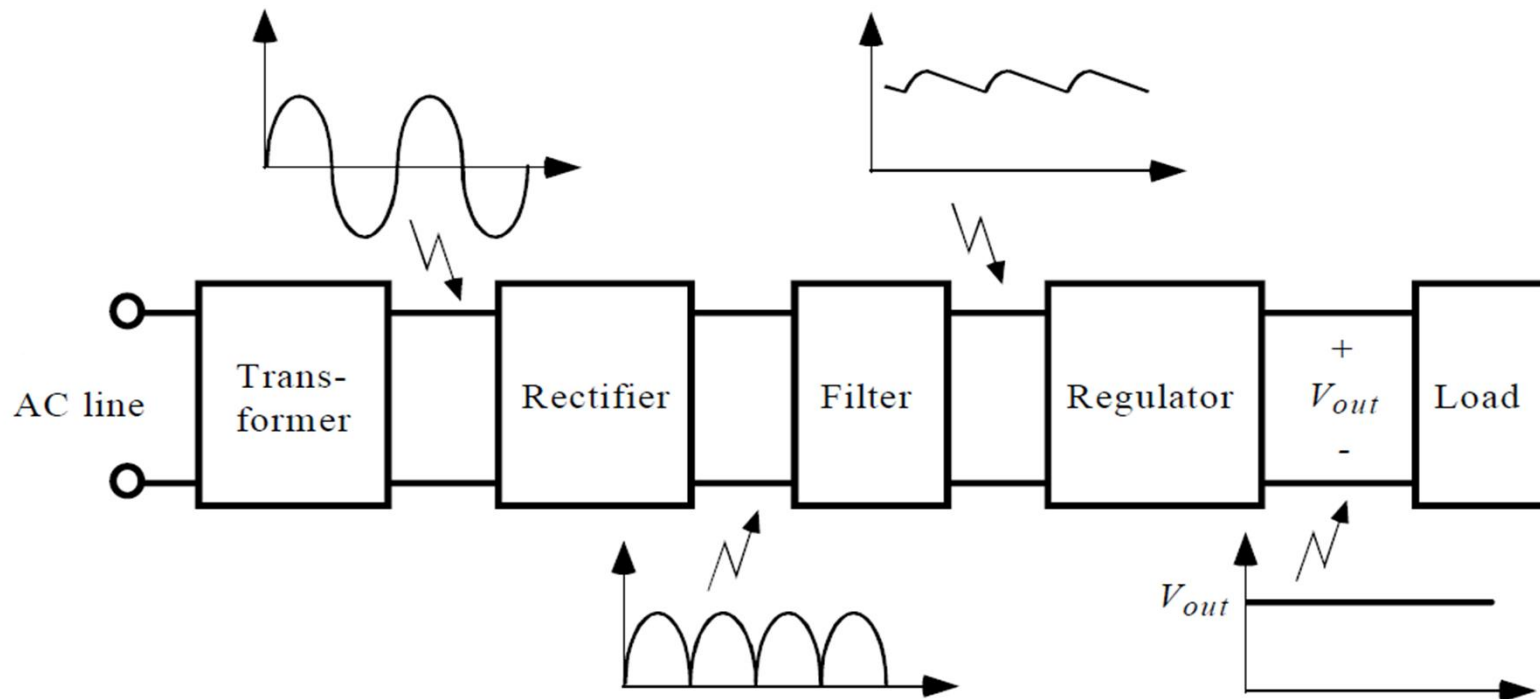- 3.1 Diode rectifier
 - 3.1.1 Half wave rectifier
 - 3.1.2 Full wave rectifier : centre tap and bridge rectifier
 - 3.1.3 Capacitive filter and DC power supply (Numerical problems)
- 3.2 Special Diodes
 - 3.2.1 Zener diode : Avalanche breakdown and Zener breakdown and characteristics.
 - 3.2.2 Zener diode as a voltage regulator
 - 3.2.3 Display devices : LED and LCD

Rectifier

A **rectifier** is an electrical device that **converts AC (alternating current) to Pulsating DC (direct current)**, which is in only one direction, a process known as **rectification**.



Basic Block Diagram of Regulated power Supply

Need of Rectification


- Every electronic circuit such as amplifiers, needs a DC power source for its operation.
- This DC voltage has to be obtained from AC supply.
- For this the AC supply has to be reduced or Stepped down first using a Step down transformer and then converted to dc by using rectifier.

Types of Rectifiers

- Half wave Rectifier
- Full wave Rectifier
- Bridge Rectifier



Half wave Rectifier

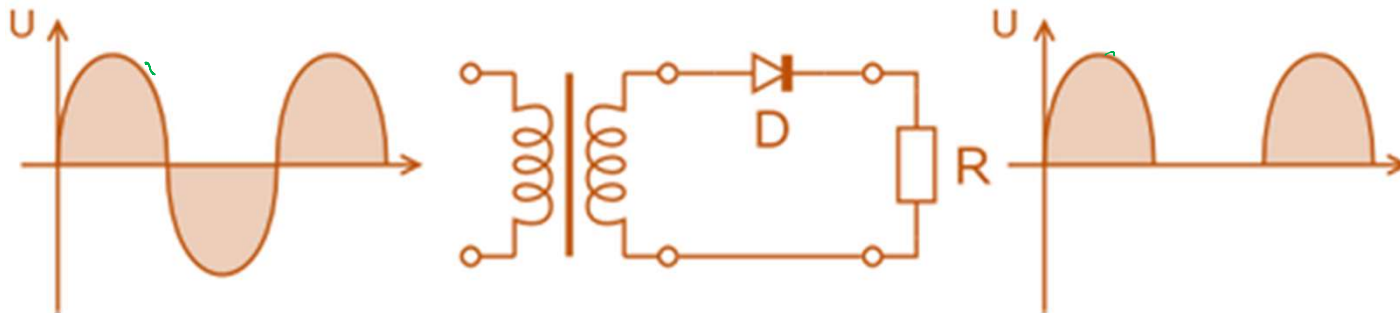- In half wave rectification, either the **positive or negative half of the AC wave is passed**, while the other half is blocked.
- Because only **one half of the input waveform reaches the output**, it is very inefficient if used for **power transfer**.





Half wave Rectifier (Cont...)

Operation

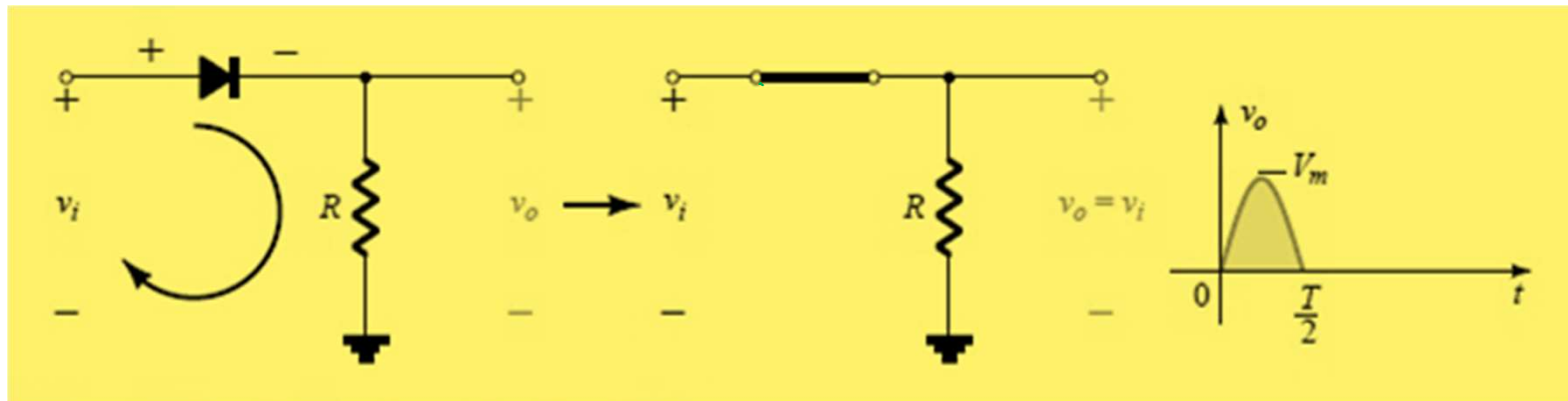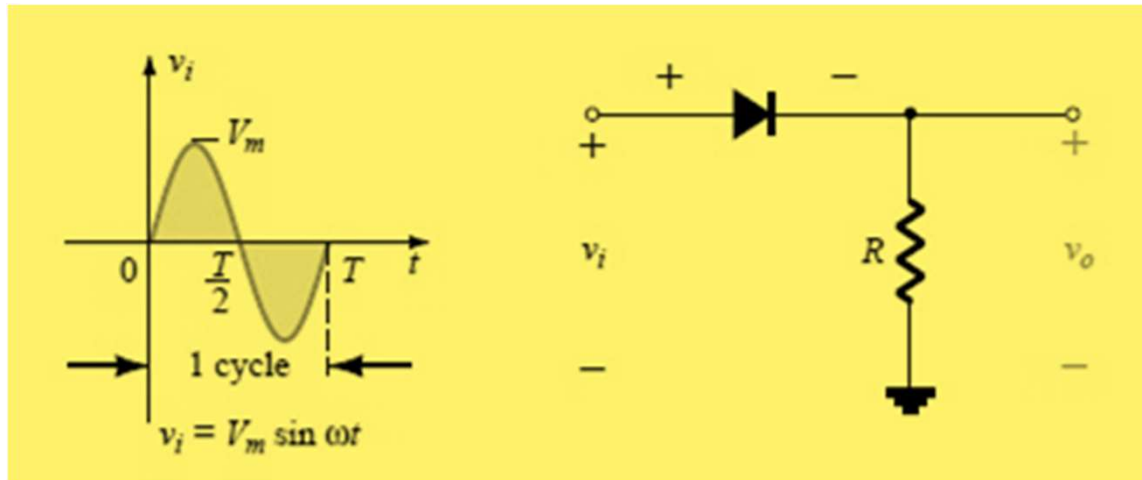

Half wave Rectifier (Cont...)

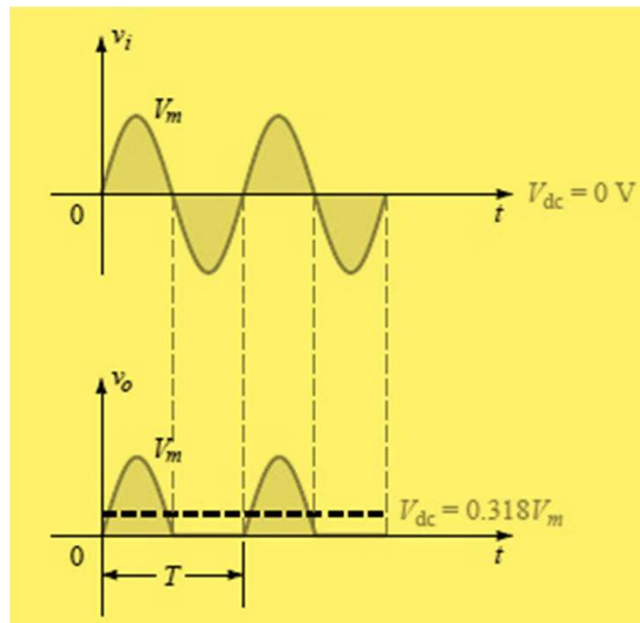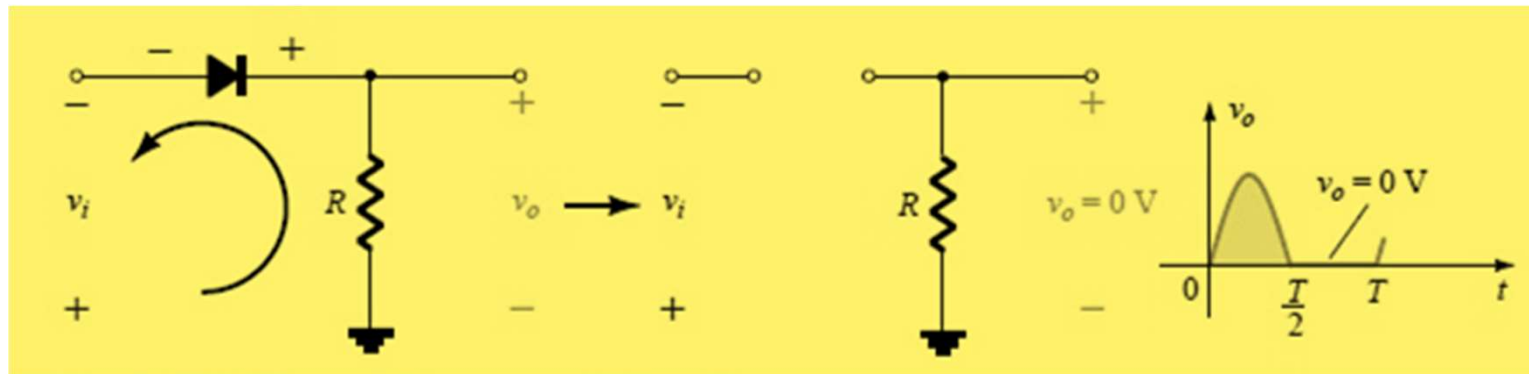

Parameters of Half Wave Rectifier

The current i_L in the diode or load R_L is given by

$$\begin{aligned} i_L &= I_m \sin \omega t && \text{when } 0 \leq \omega t \leq \pi \\ &= 0 && \text{when } \pi \leq \omega t \leq 2\pi \end{aligned}$$

1. Average or dc value of the load current:


$$I_{av} = I_{dc} = \frac{\text{area under the } i_L \text{ curve over a cycle}}{\text{base}} = \frac{\int_0^\pi i_L d(\omega t)}{2\pi}$$

$$= \frac{1}{2\pi} \int_0^\pi i_L d(\omega t) = \frac{1}{2\pi} \int_0^\pi \frac{V_m \sin \omega t d(\omega t)}{R_f + R_L}$$

$$= \frac{V_m}{2\pi(R_f + R_L)} \int_0^\pi \sin \omega t d(\omega t)$$

$$= \frac{V_m}{2\pi(R_f + R_L)} \left[-\cos \omega t \right]_0^\pi$$

$$= \frac{V_m}{2\pi(R_f + R_L)} \times 2 = \frac{V_m}{\pi(R_f + R_L)}$$

$$= \frac{I_m}{\pi} \left(\because I_m = \frac{V_m}{R_f + R_L} \right)$$


Parameters of Half Wave Rectifier (Cont...)

2. RMS value of the load current

The rms value of current flowing through the load R_L in a Half –wave rectifier is given by,

$$\begin{aligned} I_{rms} &= \sqrt{\frac{1}{2\pi} \int_0^{2\pi} i_L^2 d(\omega t)} \\ &= \sqrt{\frac{1}{2\pi} \left[\int_0^{\pi} I_m^2 \sin^2 \omega t d(\omega t) + \int_{\pi}^{2\pi} 0 d(\omega t) \right]} \\ &= \sqrt{\frac{I_m^2}{2\pi} \left[\int_0^{\pi} \frac{1 - \cos 2\omega t}{2} d(\omega t) \right]} \end{aligned}$$

$$\therefore I_{rms} = \frac{I_m}{2}$$

Parameters of HW rectifier (Cont...)

3. Ripple factor:

- **The pulsating load current i_L is the combination of dc and ripple (ac) components.** The instantaneous value of the ripple (ac) component i is the difference between the instantaneous value of i_L and the dc value of current I_{dc} . Therefore, the instantaneous value of the ripple components is given by--

$$i = i_L - I_{dc}$$

- Therefore, the rms value of the ripple (ac) current of Half – wave rectifier is given by,

$$\begin{aligned} I_{\text{ripple, rms}} &= \sqrt{\frac{1}{2\pi} \int_0^{2\pi} i^2 d(\omega t)} \\ &= \sqrt{\frac{1}{2\pi} \int_0^{2\pi} (i_L - I_{dc})^2 d(\omega t)} \\ &= \sqrt{\frac{1}{2\pi} \int_0^{2\pi} (i_L^2 + I_{dc}^2 - 2i_L I_{dc}) d(\omega t)} \end{aligned}$$

$$I_{\text{ripple, rms}} = \sqrt{i_{rms}^2 - I_{dc}^2}$$

The ripple factor γ is given by

$$\therefore \gamma = \sqrt{\left(\frac{I_{rms}}{I_{dc}}\right)^2 - 1} \quad (\text{or}) \quad \therefore \gamma = \sqrt{\left(\frac{V_{rms}}{V_{dc}}\right)^2 - 1}$$

$$\therefore \gamma = \sqrt{\left(\frac{I_m / 2}{I_m / \pi}\right)^2 - 1} = \sqrt{\left(\frac{\pi}{2}\right)^2 - 1} = 1.21$$

$$\Rightarrow \gamma = 1.21$$

Parameters of HW rectifier (Cont...)

4. Form Factor:

The ratio of the root mean square value to the average value of an alternating quantity (current or voltage) is called **Form Factor**.

$$\text{i.e. } F.F = \frac{\text{Rms value}}{\text{average value}}$$

So for hwr,

$$F.F = \frac{(I_L)_{rms}}{I_{DC}}$$
$$= \frac{\frac{I_m}{\sqrt{2}}}{\frac{I_m}{\pi}} = 1.57$$

5. Peak Inverse Voltage:

It is the maximum voltage that the rectifying diodes has to withstand, when it is reversed-biased.

$$PIV = V_m \text{ for HWR}$$

Diode operates safely if, $PIV < \text{Breakdown voltage}$

Parameters of HW rectifier (Cont...)

6. Rectification Efficiency:

$$\eta = \frac{P_{dc}}{P_i} \times 100 \% \quad \text{where } P_{dc} = I_{dc}^2 R_L$$

$$P_i = \frac{1}{2\pi} \int_0^{2\pi} v i_L d(wt) \quad \text{where } v = i_L(R_f + R_L)$$


$$= (R_f + R_L) I_{rms}^2$$

$$\eta = \left(\frac{I_{dc}^2}{I_{rms}^2} \right) \left(\frac{1}{1 + \frac{R_f}{R_L}} \right) \times 100 \%$$


$$= \frac{40.6}{1 + \frac{R_f}{R_L}}$$

Full wave Rectifier


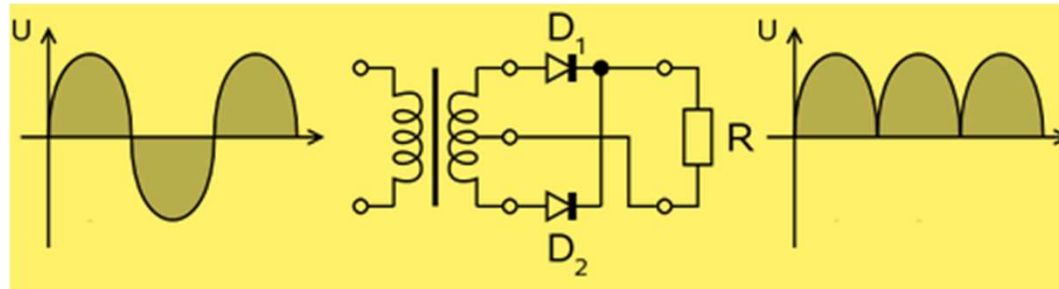
- For single-phase AC, if the transformer is center-tapped, then **two diodes back-to-back** (i.e. anodes-to-anode or cathode-to-cathode) can form a **full-wave rectifier**.




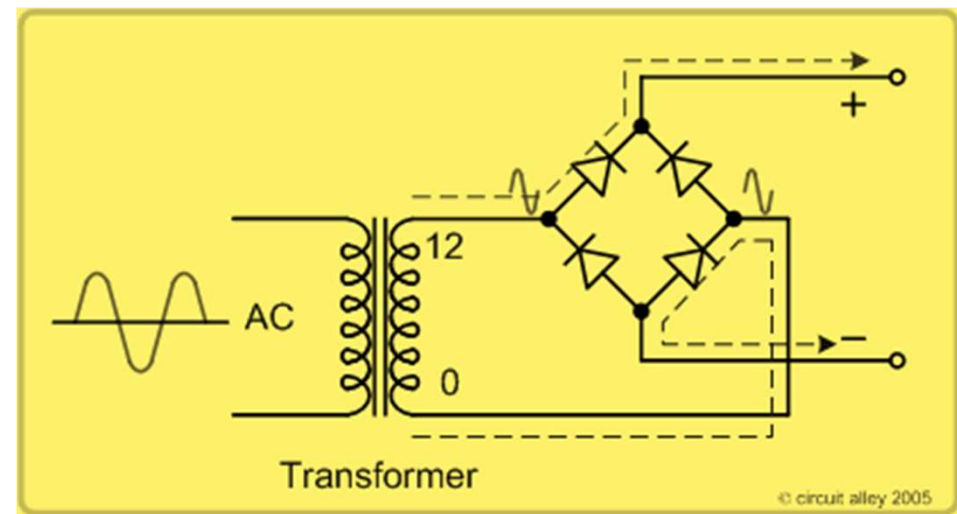
- In a circuit with a non - center tapped transformer, **four diodes** are required instead of the one needed for **half-wave rectification**.



Full wave Rectifier (Center Tapped)

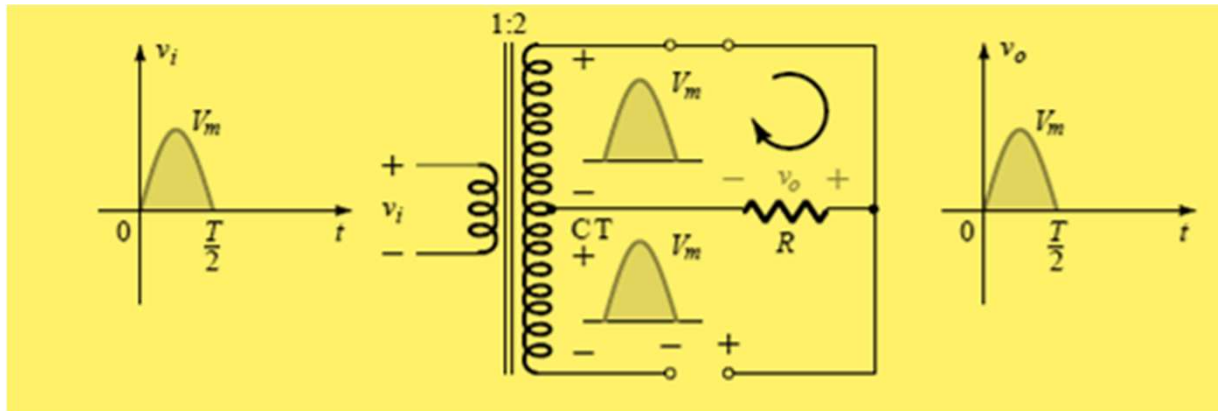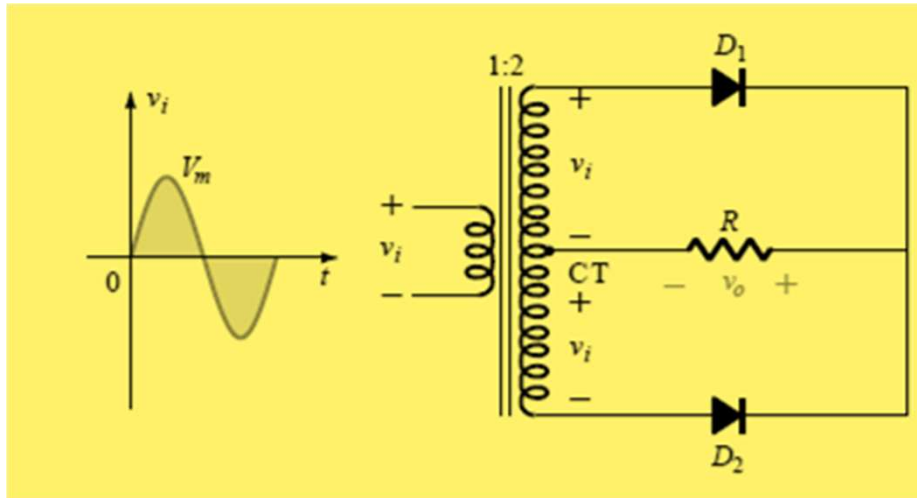


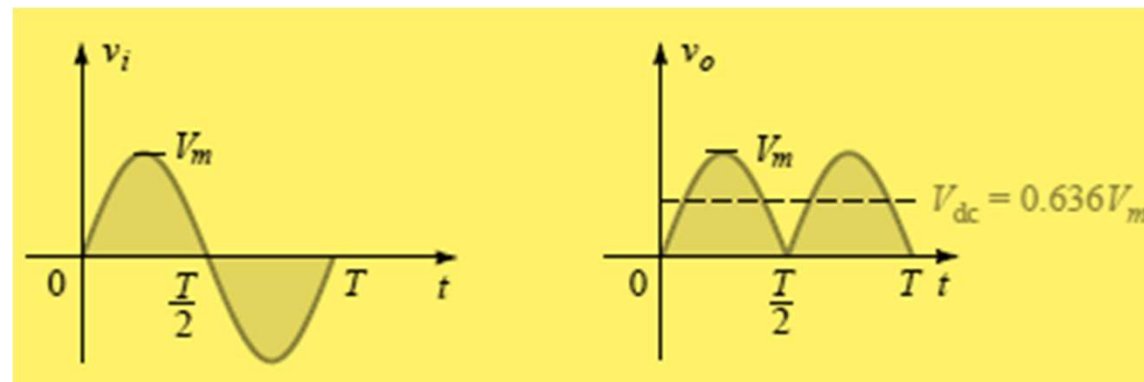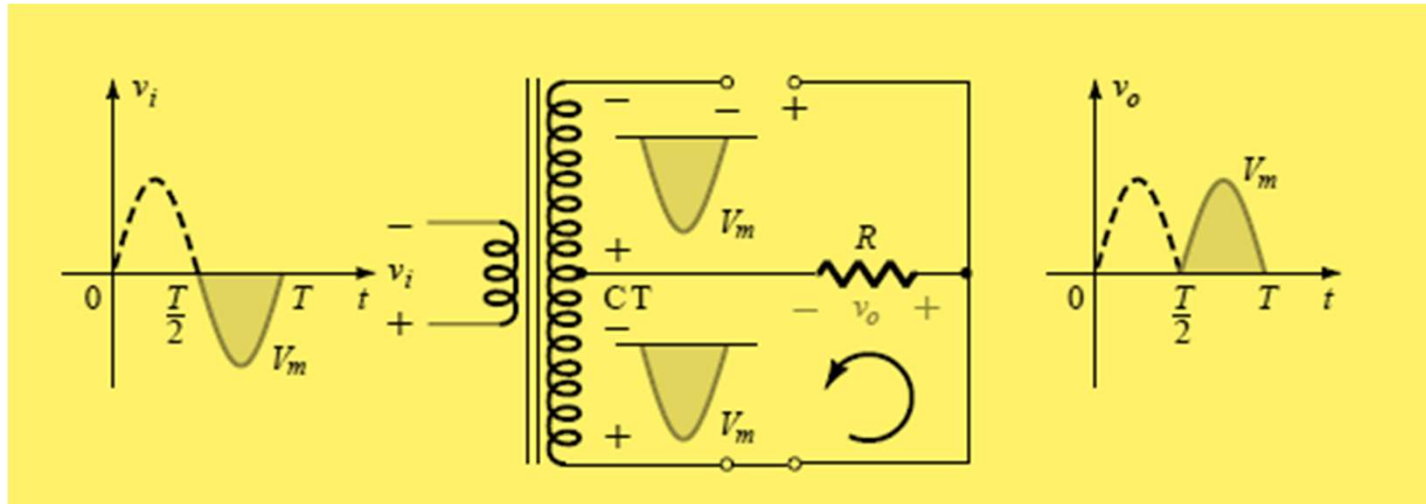Full wave Rectifier (Center Tapped) (Cont..)





Input output waveform

Full wave Rectifier (Bridge)

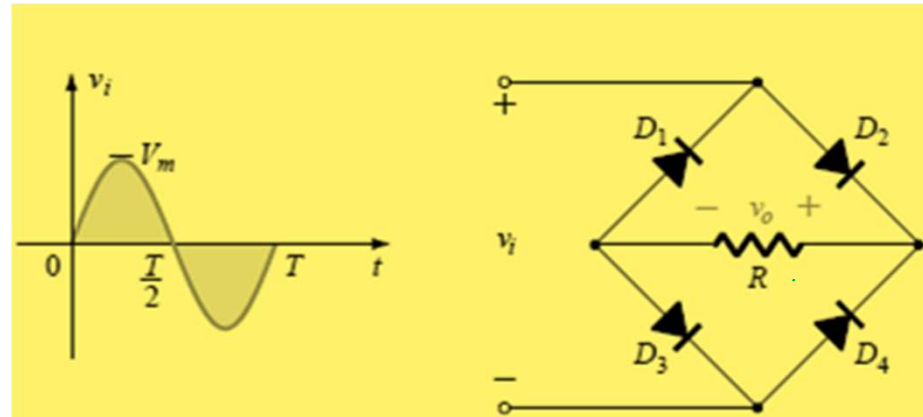


Full-wave bridge rectifier.

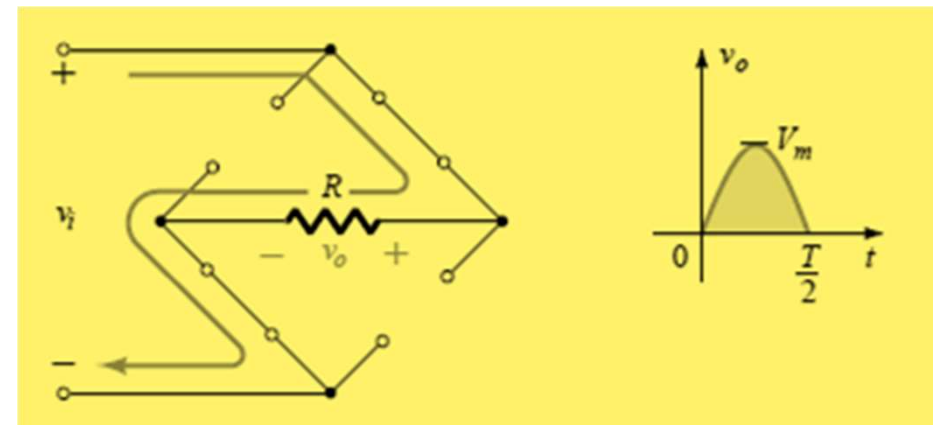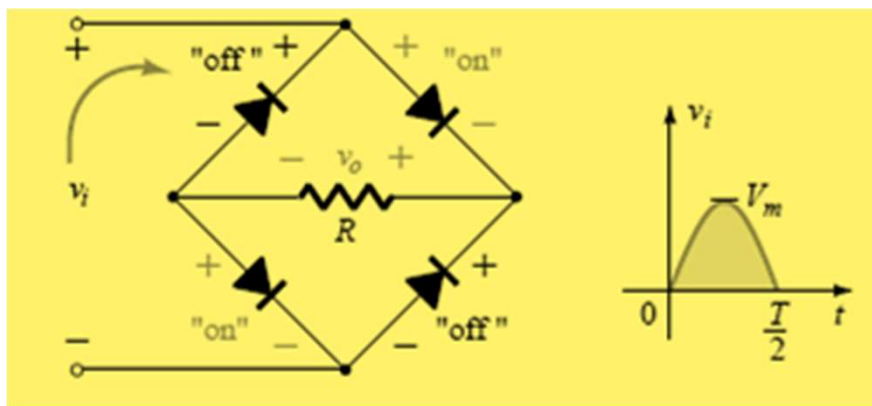


Conduction path for the positive region of v_i .

Full wave Rectifier (Bridge)

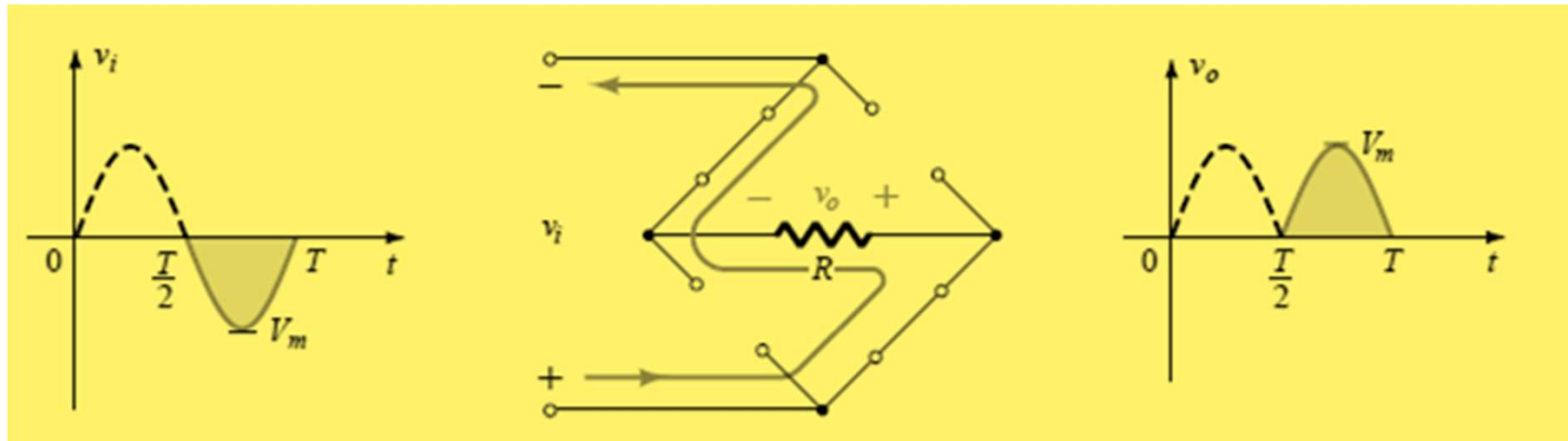

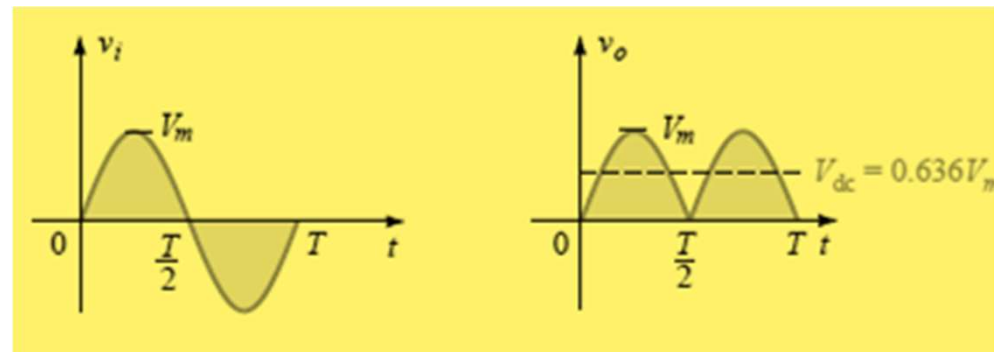Conduction path for the negative region of v_i .



Input and output waveforms for a full-wave rectifier.

Parameters of FW rectifier

The current i_L in the diode or load R_L is given by

$$\begin{aligned} i_L &= I_m \sin \omega t && \text{when } 0 \leq \omega t \leq \pi \\ &= I_m \sin \omega t && \text{when } \pi \leq \omega t \leq 2\pi \end{aligned}$$

1. Average or dc value of the load current:

$$I_{av} = I_{dc}$$

$$\begin{aligned} \text{Average Value} &= \left(\frac{1}{\pi}\right) \int_0^{\pi} I_m \sin \omega t d(\omega t) \\ &= \left(\frac{I_m}{\pi}\right) \int_0^{\pi} \sin \omega t d(\omega t) \\ &= \left(\frac{I_m}{\pi}\right) [\cos 0 - \cos \pi] \\ &= \left(2 \frac{I_m}{\pi}\right) \\ &= 0.637 I_m \end{aligned}$$

2. RMS value of the load current

$$\begin{aligned} I_{rms} &= \sqrt{\frac{1}{2\pi} \int_0^{2\pi} I_m^2 \sin^2(\omega t) d(\omega t)} \\ &= \frac{I_m}{\sqrt{2}} \end{aligned}$$

Parameters of FW rectifier (Cont...)

3. Ripple factor:

$$\begin{aligned}\text{Ripple Factor} &= \frac{\sqrt{(I_{rms})^2 - (I_{dc})^2}}{I_{dc}} \\&= \frac{\sqrt{(0.707I_m)^2 - (0.637I_m)^2}}{(0.637I_m)} \\&= \frac{\sqrt{(0.707I_m)^2 - (0.637I_m)^2}}{(0.637I_m)} \\&= 0.482\end{aligned}$$

4. Form Factor:

The ratio of the root mean square value to the average value of an alternating quantity (current or voltage) is called **Form Factor**.

$$\text{Form Factor} = \frac{I_{r.m.s}}{I_{av}} = \frac{I_m / \sqrt{2}}{2I_m / \pi} = \frac{\pi I_m}{2\sqrt{2}I_m} = 1.11$$

Parameters of FW rectifier (Cont...)

5. Peak Inverse Voltage:

It is the maximum voltage that the rectifying diodes has to withstand, when it reversed-biased.

$$PIV = 2V_m \text{ for FWR (Center Tapped)}$$

$$PIV = V_m \text{ for FWR (Bridge)}$$


Diode operates safely if, $PIV < \text{Breakdown voltage}$

6. Rectification Efficiency:


$$\eta = \left(\frac{I_{dc}^2}{I_{rms}^2} \right) \left(\frac{1}{1 + \frac{R_f}{R_L}} \right) \times 100 \%$$
$$= \frac{81.2}{1 + \frac{R_f}{R_L}}$$

Filter Circuits

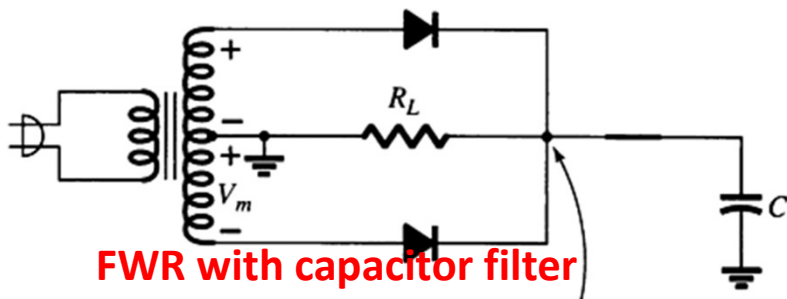- The output from the rectifier section is a pulsating DC.
- The filter circuit reduces the peak-to-peak pulses to a small ripple voltage.
- The commonly used filters are a
Capacitor Filter


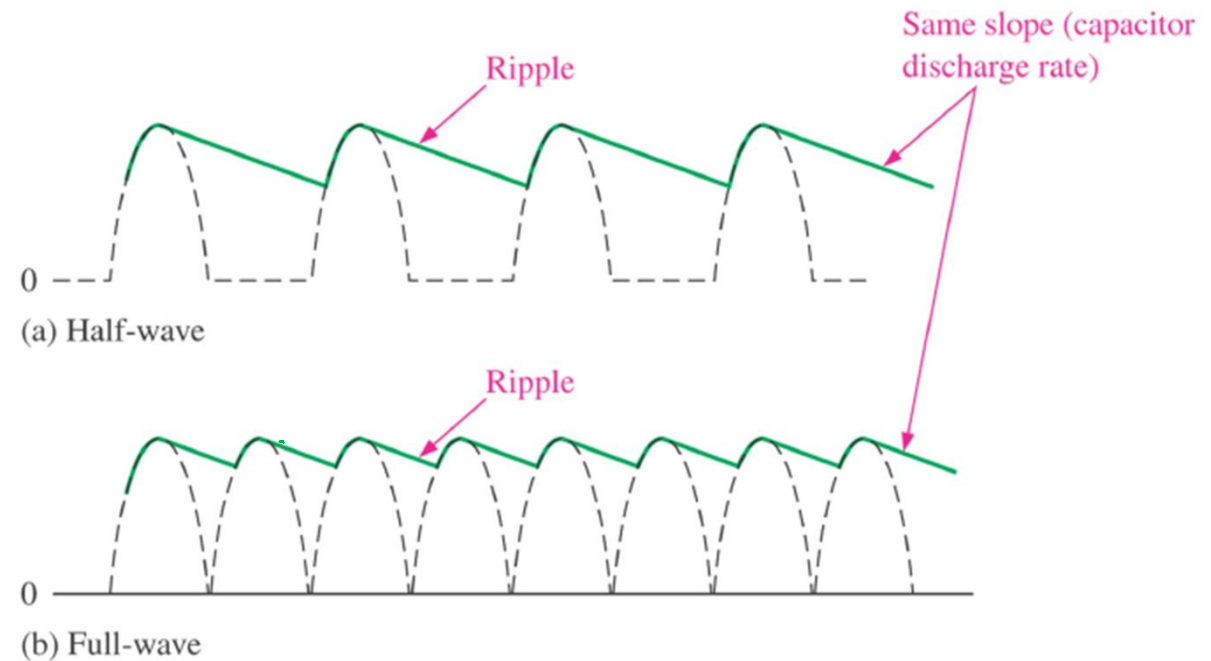
$$\text{Ripple voltage (peak to peak)} = \frac{V_m}{f R_L C}$$




Regulator

- A voltage regulator regulates the voltage, regardless of the adjustments in the input voltage or connected load.


❖ Zener Diode as a voltage regulator:

The zener diode is used to provide an output reference voltage that is stable despite changes in input voltage

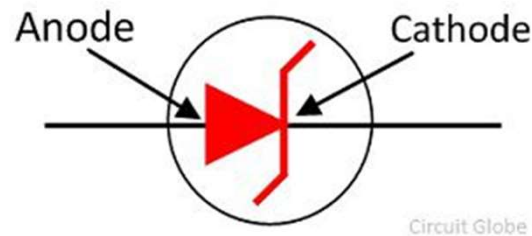
- Used as a reference in regulated power supplies
- The zener diode is designed for operation in the reverse breakdown region, where the voltage remains almost constant over a wide range of reverse current values



Zener Diode

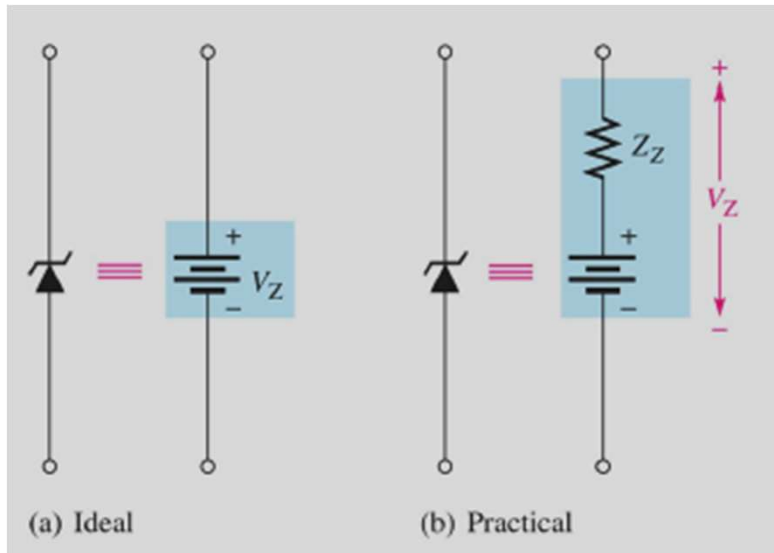


Zener diode equivalent circuit

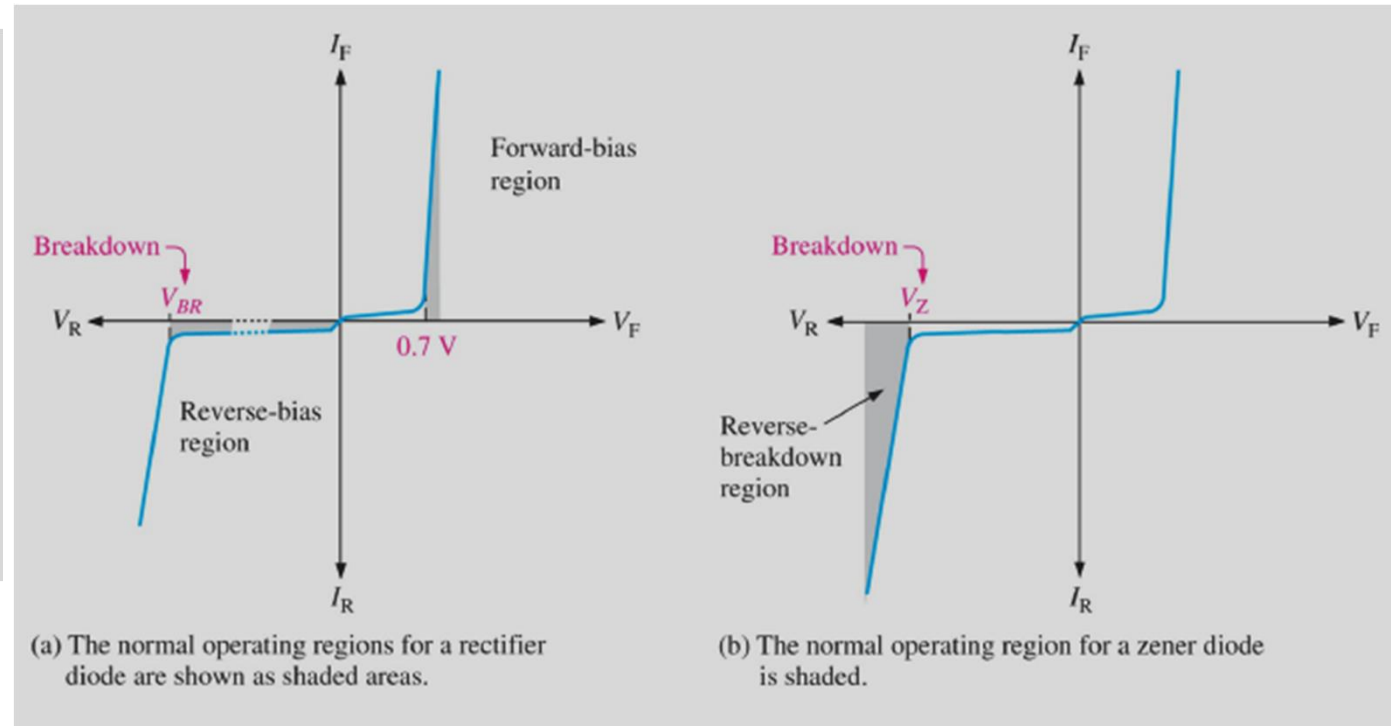

Diode V-I characteristic

Zener Regulator

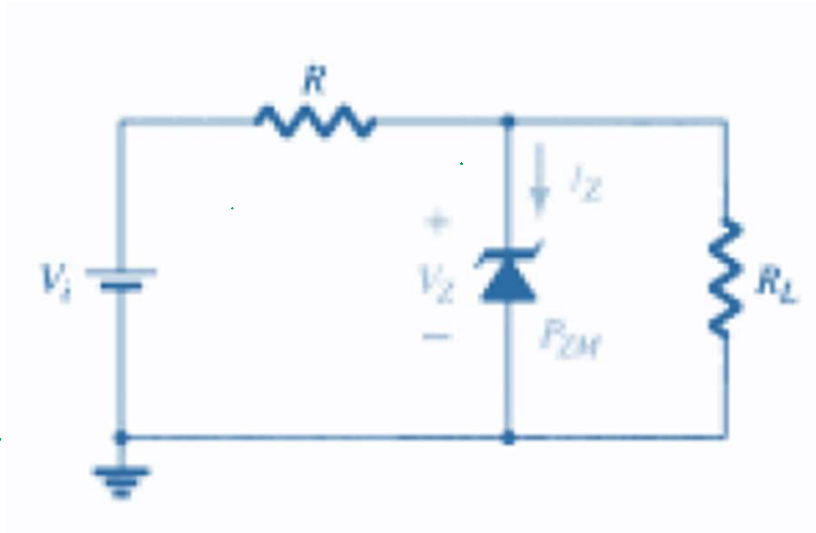

If $V \geq V_Z$, the Zener diode is “on”

$$V_L = V_Z$$

$$I_R = I_Z + I_L$$



$$I_Z = I_R - I_L$$

$$I_L = \frac{V_L}{R_L} \quad \text{and} \quad I_R = \frac{V_R}{R} = \frac{V_i - V_L}{R}$$

The power dissipated by the Zener diode is determined by

$$P_Z = V_Z I_Z$$

If $V < V_Z$, the diode is “off”

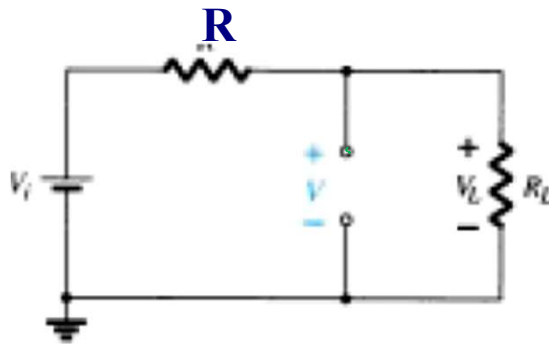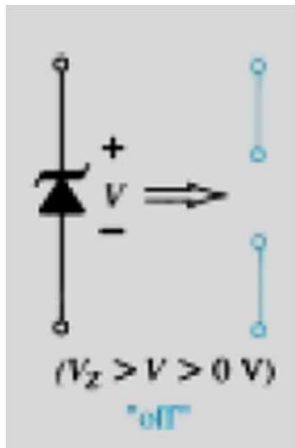

$$V = V_L = \frac{R_L V_i}{R + R_L}$$

$$V_i > V_Z (1 + R/R_L) \Rightarrow V_o = V_Z$$


Fixed V_i , Variable R_L

To find minimum R_L

$$V_L = V_Z = \frac{R_L V_i}{R_L + R}$$

$$R_{L_{\min}} = \frac{R V_Z}{V_i - V_Z}$$
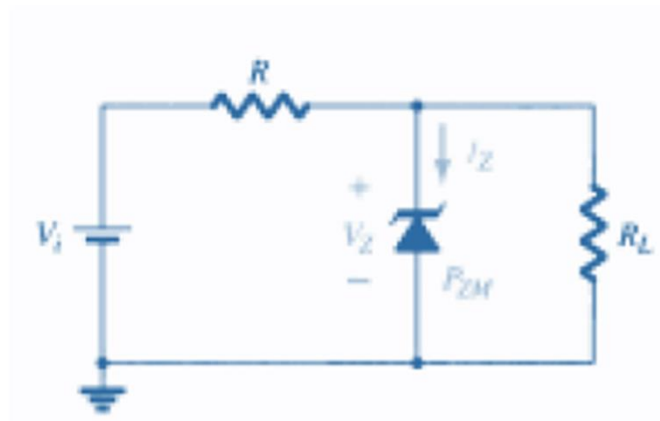
$$I_{L_{\max}} = \frac{V_L}{R_L} = \frac{V_Z}{R_{L_{\min}}}$$



Once the diode is in the “on” state, the voltage across R remains fixed at

$$V_R = V_i - V_Z$$

and I_R remains fixed at

$$I_R = \frac{V_R}{R}$$

The Zener current

$$I_Z = I_R - I_L$$

$$I_{L_{\min}} = I_R - I_{ZM}$$

$$R_{L_{\max}} = \frac{V_Z}{I_{L_{\min}}}$$

Fixed R_L , Variable V_i

The minimum turn-on voltage $V_i = V_{i_{\min}}$ is determined by

$$V_L = V_Z = \frac{R_L V_i}{R_L + R}$$

$$V_{i_{\min}} = \frac{(R_L + R)V_Z}{R_L}$$


The maximum value of V_i is limited by the maximum Zener current I_{ZM} . Since $I_{ZM} = I_R - I_L$,


$$I_{R_{\max}} = I_{ZM} + I_L$$

Since I_L is fixed at V_Z/R_L and I_{ZM} is the maximum value of I_Z , the maximum V_i is defined by

$$V_{i_{\max}} = V_{R_{\max}} + V_Z$$

$$V_{i_{\max}} = I_{R_{\max}} R + V_Z$$

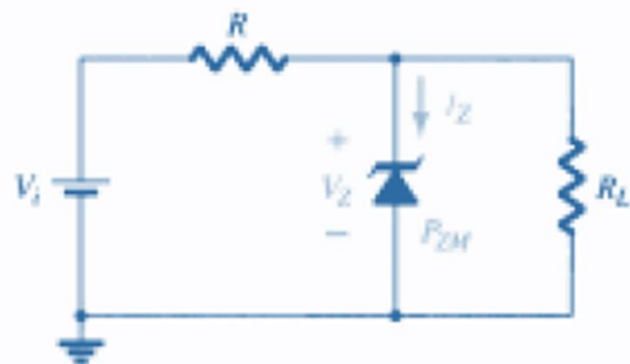

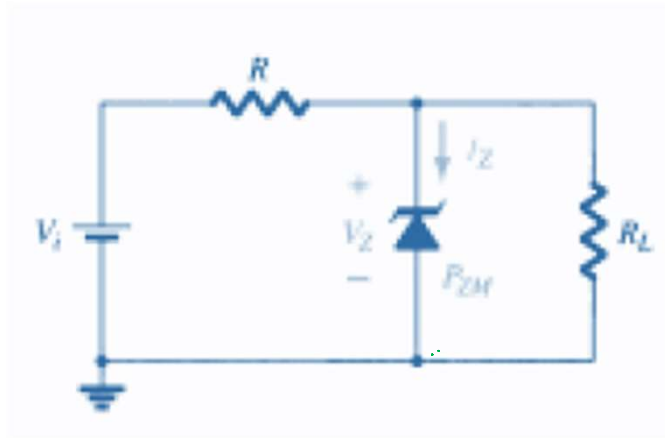

$$R = 220\Omega$$

$$V_Z = 10V$$

$$P_{Z \max} = 400 \text{ mW}$$

$$V_i = 20 \text{ V}$$

- i. Find V_L , I_L , I_Z , and I_R if $R_L = 180\Omega$
- ii. Repeat if $R_L = 470\Omega$
- iii. Find R_L that will establish max power
- iv. Find the min. R_L to ensure that Zener diode is ON.

i.

$$V = V_L = \frac{R_L V_i}{R + R_L} = 9V$$

If $V < V_Z$, the diode is "off"

$$I_Z = 0$$

$$I_L = I_R = 20 / (220 + 180) = 50 \text{ mA}$$

ii.

$$V = V_L = \frac{R_L V_i}{R + R_L} = 13.62V$$

If $V \geq V_Z$, the Zener diode is "on"

$$V_L = V_Z = 10V \quad I_L = V_L / R_L = 10 / 470 = 21.28 \text{ mA}$$

$$V_R = 20 - 10 = 10V \quad I_R = V_R / R = 10 / 220 = 45.45 \text{ mA}$$

$$I_Z = I_R - I_L = 24.17 \text{ mA}$$

iii. $P_z \text{ max} = 400 \text{ mW} = V_z \times I_z = 10 \times I_z, \text{ max}$

$$I_z, \text{ max} = 40 \text{ mA}$$

$$I_L, \text{ min} = I_R - I_z, \text{ max} = 45.45 - 40 = 5.45 \text{ mA}$$

$$R_L = V_L / I_L, \text{ min} = 10 \text{ V} / 5.45 \text{ mA} = 1834.86 \text{ Ohm}$$

iv.
$$R_{L_{\text{min}}} = \frac{RV_Z}{V_i - V_Z} = 220 \text{ ohm}$$


Voltage Regulation:

Line regulation is a measure of the circuit's ability to maintain the specified output voltage with varying input voltage. Line regulation is defined as

$$\text{Line regulation} = \delta V_o / \delta V_i$$

Load regulation is a measure of the circuit's ability to maintain the specified output voltage under varying load conditions. Load regulation is defined as
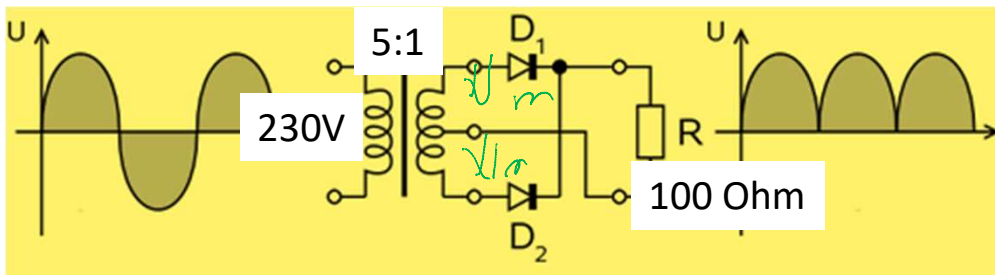
$$\text{Load regulation} = \delta V_o / \delta I_o$$



Find DC voltage

Centre Tap Rectifier


RMS secondary voltage = $230 \times 1/5 = 46\text{V}$

Max or peak voltage across secondary = $46\sqrt{2} = 65\text{V}$

Max voltage appearing across half secondary (V_m) = $65/2 = 32.5\text{ V}$

$I_{DC} = 2I_m/\pi = 2V_m/\pi R_L$

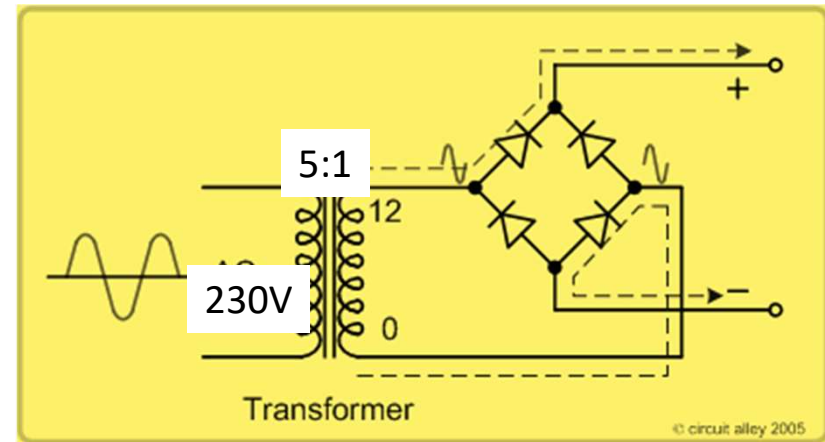$V_{DC} = I_{DC} \times R_L = 2V_m/\pi = 20.7\text{V}$



Bridge Rectifier

$V_m = 65\text{V}$

$V_{DC} = I_{DC} \times R_L = 2V_m/\pi = 41.4\text{V}$